

# 2 channel Amplitude Modulator

By: Chris Bake

- [Simplest 2 Channel Modulator](#)

# Simplest 2 Channel Modulator

20220625\_234330.jpg

Image not found or type unknown

20220625\_234338.jpg

Image not found or type unknown

Mixing effects of true analog amplitude modulation using 2 pots and 2 opto-couplers

<https://www.youtube.com/embed/NVPALWhoxnY>