

# Simplest 2 Channel Modulator

[20220625\\_234330.jpg](#)

[20220625\\_234338.jpg](#)

Mixing effects of true analog amplitude modulation using 2 pots and 2 opto-couplers

<https://www.youtube.com/embed/NVPALWhoxnY>

---

Revision #2

Created 2022-06-26 03:39:59 UTC by Chris Bake

Updated 2022-06-26 03:45:25 UTC by Chris Bake