

Advanced Topics

- [PLL Control](#)
- [Harmonic Analysis](#)
- [Transformer Coupling](#)
- [Energy Efficiency](#)
- [Experimental Validation](#)
- [Understanding Resonant Action in the Water Fuel Cell](#)

PLL Control

PLL-Based Frequency Control

Phase-Locked Loop (PLL) circuits can automatically track and maintain resonance in VIC systems, compensating for drift due to temperature changes, water level variations, and other factors. This page covers PLL fundamentals and their application to VIC circuits.

Why PLL Control?


VIC resonant frequency can drift during operation due to:

Factor	Effect on f_0	Typical Drift
Water temperature rise	f_0 increases (ϵ_r drops)	+0.2%/°C
Gas bubble formation	f_0 increases (C drops)	+2-10%
Water level change	f_0 changes (C changes)	Variable
Core temperature rise	f_0 may shift (μ changes)	±1%

A PLL can continuously adjust the drive frequency to maintain optimal resonance despite these variations.

PLL Fundamentals

Basic PLL Components:

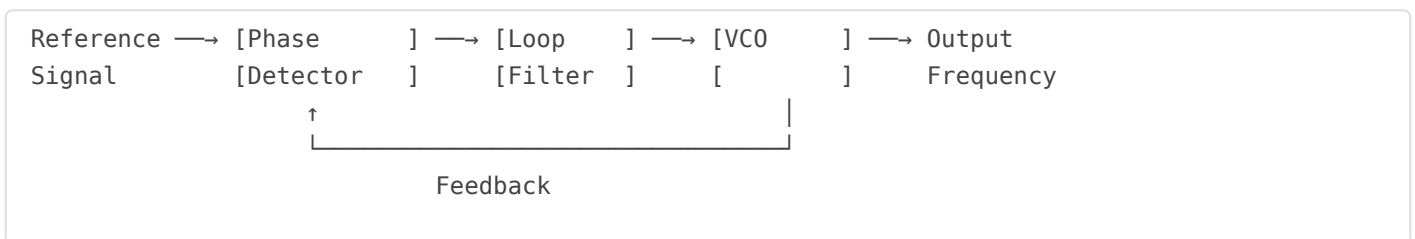


Components Explained:

- **Phase Detector:** Compares phase of two signals, outputs error voltage
- **Loop Filter:** Averages error signal, sets response speed
- **VCO:** Voltage-Controlled Oscillator, frequency varies with input voltage

PLL for VIC Resonance Tracking

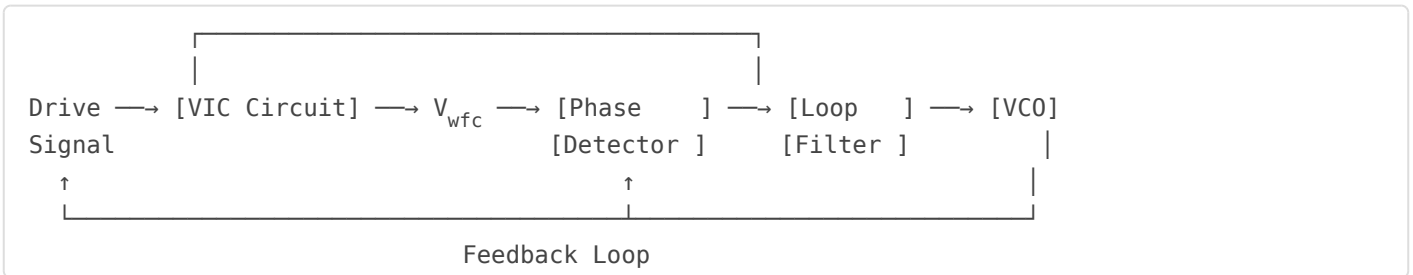For VIC applications, the PLL tracks the resonant frequency by sensing the phase relationship between drive signal and cell response:



Phase Detection Methods

Method	Description	Pros/Cons
XOR Phase Detector	Digital XOR of drive and response	Simple, but needs square waves
Analog Multiplier	Multiply drive × response	Works with sinusoids, more complex
Zero-Crossing Detector	Compare zero-crossing times	Digital-friendly, noise sensitive
I/Q Demodulation	Quadrature phase detection	Most accurate, most complex

Resonance Tracking Logic

At resonance, the phase relationship between drive current and WFC voltage is 0°:

Phase vs. Frequency:

- $f < f_0$: V leads I (capacitive), phase $> 0^\circ$
- $f = f_0$: V and I in phase, phase = 0°
- $f > f_0$: V lags I (inductive), phase $< 0^\circ$

Control Law:

- If phase $> 0^\circ$: Increase frequency (move toward resonance)
- If phase $< 0^\circ$: Decrease frequency (move toward resonance)
- If phase $\approx 0^\circ$: Maintain frequency (at resonance)

Loop Filter Design

The loop filter determines how quickly the PLL responds to changes:

Parameter	Fast Response	Slow Response
Tracking speed	Quick adaptation	Slow adaptation
Noise rejection	Poor	Good
Stability	May oscillate	More stable
Best for	Rapid changes	Gradual drift

Design Tip: For VIC applications, a medium-speed loop (bandwidth ~ 100 -500 Hz) usually works well. Fast enough to track bubble-induced changes, slow enough to reject noise.

VCO Implementation

The VCO generates the variable-frequency drive signal:


Common VCO Options:

- **555 Timer VCO:** Simple, wide frequency range, moderate stability
- **74HC4046 PLL IC:** Integrated PLL with VCO, easy to use
- **DDS (Direct Digital Synthesis):** Precise frequency control, programmable
- **Microcontroller PWM:** Software-adjustable, flexible

VCO Requirements:

- Frequency range covering expected $f_0 \pm$ drift range
- Linear frequency vs. voltage response
- Low noise and jitter
- Fast frequency settling

Complete PLL-VIC System

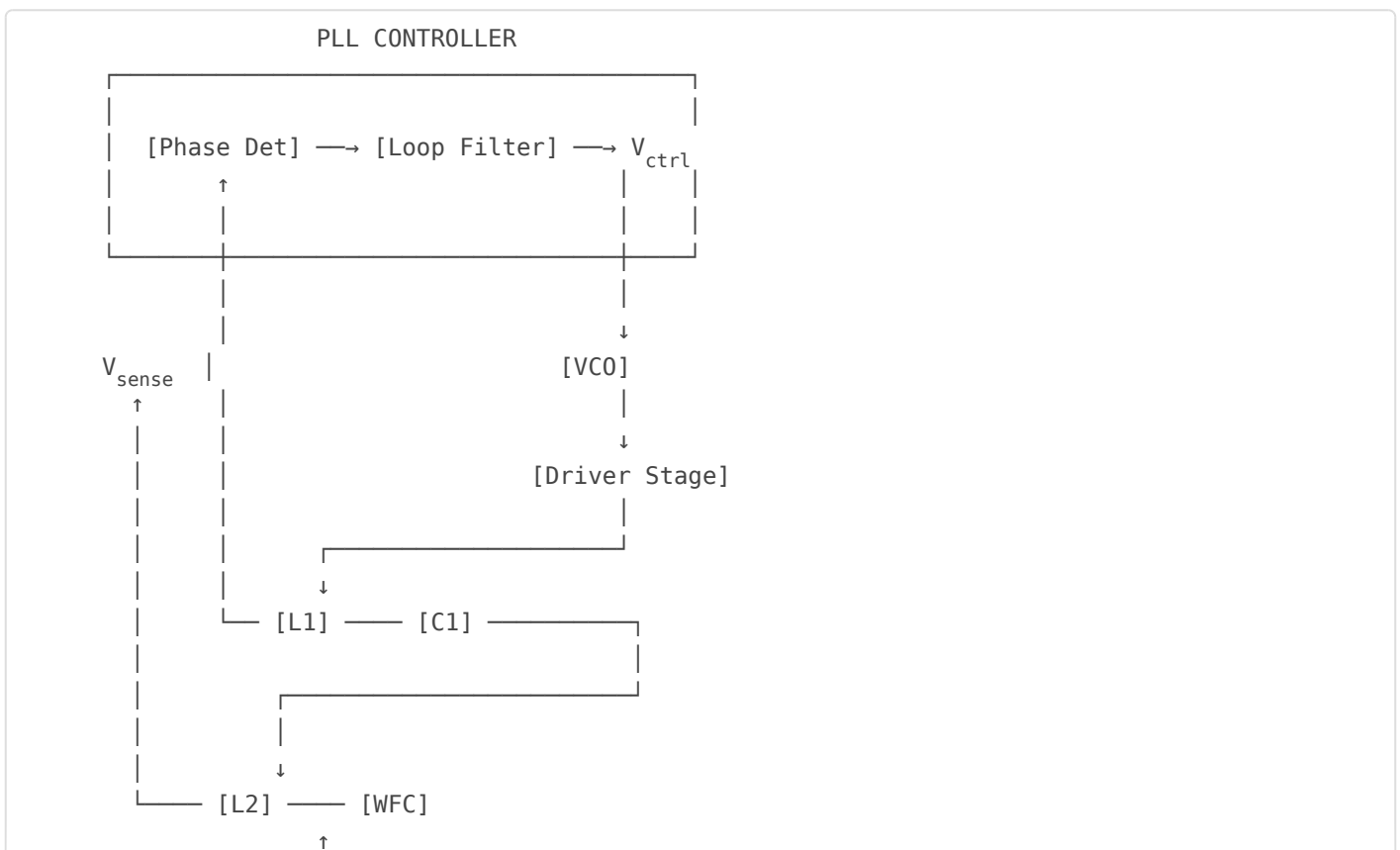

Practical Considerations

Startup Sequence:

1. Initialize VCO near expected f_0
2. Enable PLL with wide bandwidth initially
3. Wait for lock indication
4. Reduce bandwidth for stable operation

Lock Detection:

Monitor loop filter output—stable voltage indicates lock. Large variations indicate searching or loss of lock.

Capture Range:

PLL can only lock if initial frequency is within "capture range." If f_0 drifts too far, may need frequency sweep to re-acquire.

Alternatives to PLL

Method	Description	When to Use
Fixed Frequency	No tracking, fixed drive	Stable systems, low Q
Frequency Sweep	Periodically sweep through range	Testing, characterization
Peak Detector	Track amplitude maximum	Simpler than phase tracking
Self-Oscillation	Circuit sets own frequency	Simple, but less control

VIC Matrix Calculator Note: The VIC5 PLL module provides calculations for PLL component selection, including VCO tuning range, loop filter values, and expected tracking bandwidth. Use

these calculations when implementing automatic resonance tracking.

Next: Harmonic Analysis →

Harmonic Analysis

Harmonic Analysis

VIC circuits are typically driven by non-sinusoidal waveforms (pulses, square waves), which contain harmonics. Understanding how these harmonics interact with the resonant circuit is important for predicting actual performance and potential interference effects.

Fourier Analysis Basics

Any periodic waveform can be decomposed into a sum of sinusoids:

Fourier Series:

$$f(t) = a_0 + \sum [a_n \cos(n\omega t) + b_n \sin(n\omega t)]$$

Where $n = 1, 2, 3, \dots$ are the harmonic numbers ($n=1$ is fundamental)

Harmonic Content of Common Waveforms

Square Wave

50% duty cycle square wave contains only odd harmonics:

$$v(t) = (4V_{pk}/\pi) [\sin(\omega t) + (1/3)\sin(3\omega t) + (1/5)\sin(5\omega t) + \dots]$$

Harmonic	Frequency	Relative Amplitude
1st (fundamental)	f	100%
3rd	3f	33.3%
5th	5f	20%

Harmonic	Frequency	Relative Amplitude
7th	7f	14.3%

Pulse Train (Variable Duty Cycle)

Pulse train with duty cycle D contains both odd and even harmonics:


$$a_n = (2V_{pk}/n\pi) \times \sin(n\pi D)$$

Effect of Duty Cycle:

- **D = 50%:** Only odd harmonics (even harmonics cancel)
- **D = 25%:** Strong 2nd harmonic, weak 4th
- **D = 33%:** No 3rd harmonic (3rd harmonic null)
- **Narrow pulse:** Wide harmonic spectrum, many significant harmonics

Resonant Circuit Response to Harmonics

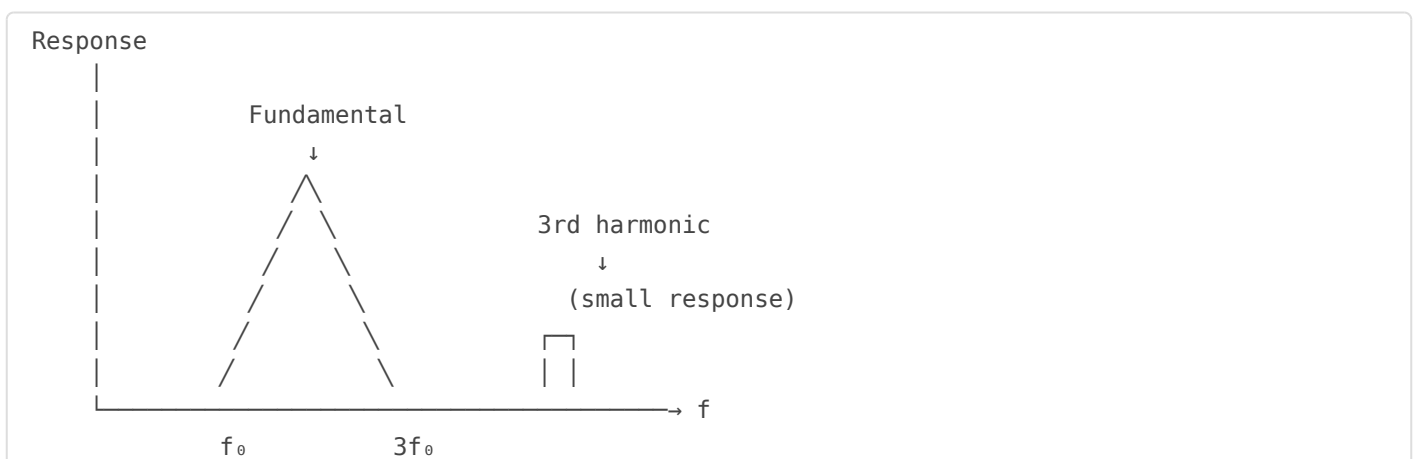A resonant circuit acts as a bandpass filter. It responds most strongly to frequencies near f_0 :



Response at Harmonic Frequencies:

$$H(nf) = 1 / \sqrt{[1 + Q^2(n - 1/n)^2]}$$

For high Q circuits, harmonics far from f_0 are strongly attenuated.

Example ($Q=50$, $f_0=10$ kHz):

- At 10 kHz (1st): Response = 100%
- At 30 kHz (3rd): Response $\approx 0.6\%$
- At 50 kHz (5th): Response $\approx 0.2\%$

Harmonic Resonance

If a harmonic happens to fall near f_0 , it can cause problems or opportunities:

Scenario	Effect	Action
Drive at f_0	Fundamental resonates	Normal operation
Drive at $f_0/2$	2nd harmonic resonates	May be useful or problematic
Drive at $f_0/3$	3rd harmonic resonates	Subharmonic driving
Harmonic hits SRF	Choke self-resonates	Avoid—causes problems

Sub-Harmonic Driving

It's possible to drive the circuit at a sub-multiple of f_0 and let a harmonic excite resonance:

Example: 3rd Harmonic Drive

- Circuit resonance: $f_0 = 30$ kHz
- Drive frequency: $f_{\text{drive}} = 10$ kHz
- 3rd harmonic of drive (30 kHz) excites resonance

Advantages:

- Lower switching frequency (easier on semiconductors)
- Different pulse characteristics
- May interact differently with WFC

Disadvantages:

- Harmonic has lower amplitude than fundamental
- Reduced efficiency (energy in unused harmonics)
- More complex analysis


Pulse Shaping for Harmonic Control


Adjusting pulse shape can control harmonic content:

Technique	Effect
Slower edges (rise/fall time)	Reduces high-order harmonics
Duty cycle = $1/n$	Eliminates nth harmonic
Trapezoidal waveform	Controlled harmonic rolloff
Sine wave drive	No harmonics (pure fundamental)

Harmonic Interaction with Multiple Resonances

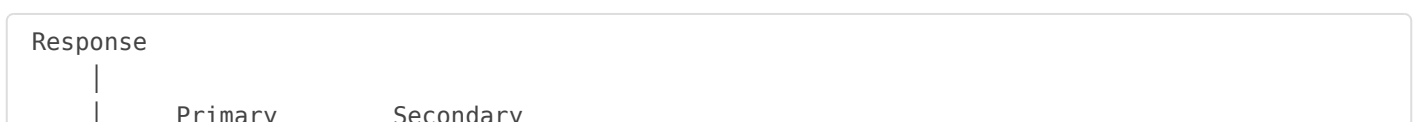In dual-resonant VIC (primary + secondary), harmonics may interact with both:



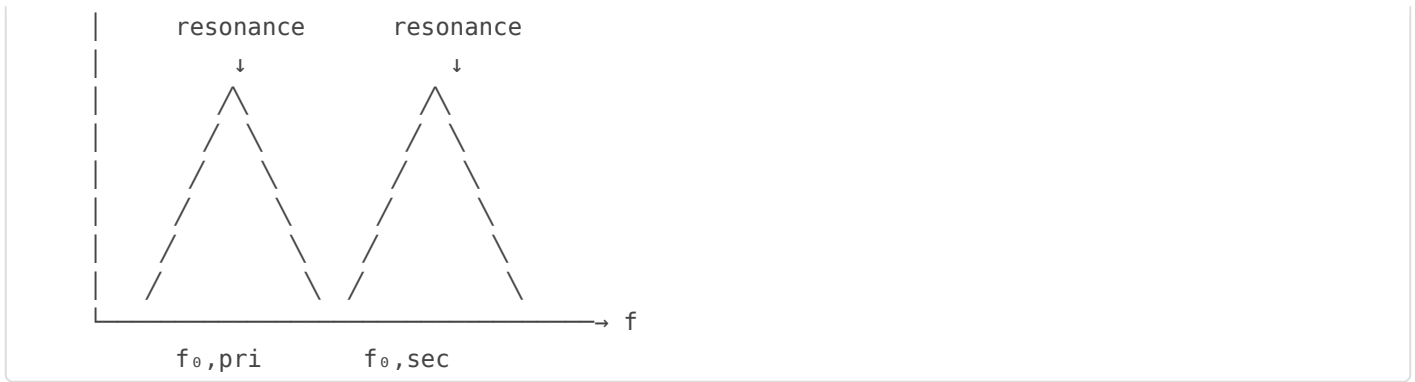

If $f_{0,sec} = 3 \times f_{0,pri}$, then:

- Fundamental drives primary resonance
- 3rd harmonic drives secondary resonance
- This is sometimes called "harmonic matching"

Practical Harmonic Considerations

EMI Concerns:

Harmonics can cause electromagnetic interference. Shield appropriately and consider filtering if needed.

Measurement:

Use an oscilloscope with FFT function or spectrum analyzer to view harmonic content of your signals.

Design Rule:

For clean resonance, ensure no significant harmonics fall within the passband ($f_0 \pm f_0/Q$) of unintended resonances.

Harmonic Analysis in VIC Matrix Calculator

Calculator Feature: The simulation can show frequency response across a range that includes harmonics. When analyzing a design, check whether any harmonics of your drive frequency fall near the circuit's resonant points or SRF values.

Next: Transformer Coupling Effects →

Transformer Coupling

Transformer Coupling Effects

In VIC circuits, the primary (L1) and secondary (L2) chokes may be magnetically coupled, either intentionally (bifilar winding) or unintentionally (proximity). This coupling significantly affects circuit behavior and must be understood for accurate analysis.

Magnetic Coupling Fundamentals

When two inductors share magnetic flux, they become coupled:

Mutual Inductance:

$$M = k \times \sqrt{L_1 \times L_2}$$


Where k is the coupling coefficient ($0 \leq k \leq 1$)

Coupling Coefficient:

- **$k = 0$** : No coupling (independent inductors)
- **$k = 0.01-0.1$** : Loose coupling (separate cores, some proximity)
- **$k = 0.5-0.8$** : Moderate coupling (shared core, separate windings)
- **$k = 0.95-0.99$** : Tight coupling (bifilar, interleaved windings)
- **$k = 1$** : Perfect coupling (theoretical ideal transformer)

Coupled Inductor Equivalent Circuit

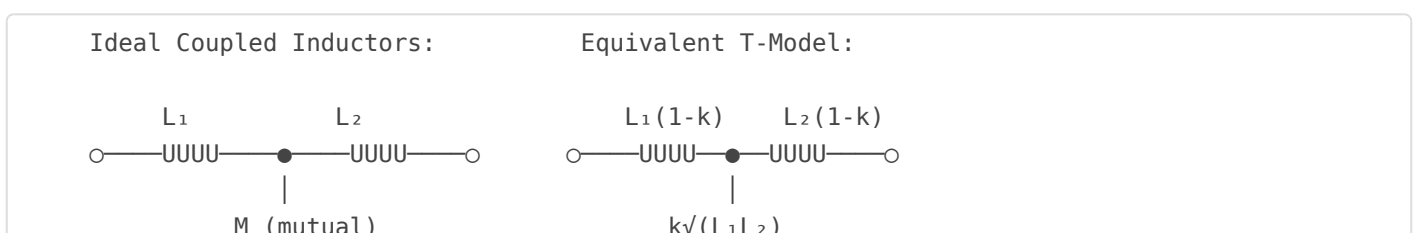Coupled inductors can be modeled as a transformer with leakage inductances:





T-Model Components

Component	Formula	Represents
L_{leak1}	$L_1(1-k)$	Primary leakage inductance
L_{leak2}	$L_2(1-k)$	Secondary leakage inductance
L_m	$k\sqrt{L_1L_2}$	Magnetizing inductance

Effect on VIC Circuit Behavior

Resonant Frequency Shifts

Coupling changes the effective inductances seen by each resonant tank:

Without Coupling ($k=0$):

$$f_{pri} = 1/\sqrt{L_1 C_{wfc}}$$
$$f_{sec} = 1/\sqrt{L_2 C_{wfc}}$$

With Coupling:


The system has two coupled resonant modes. The frequencies split into:

$$f_{+}, f_{-} = \text{function of } L_1, L_2, C_{wfc}, \text{ and } k$$

Exact formulas are complex—use simulation for accurate prediction.

Mode Splitting

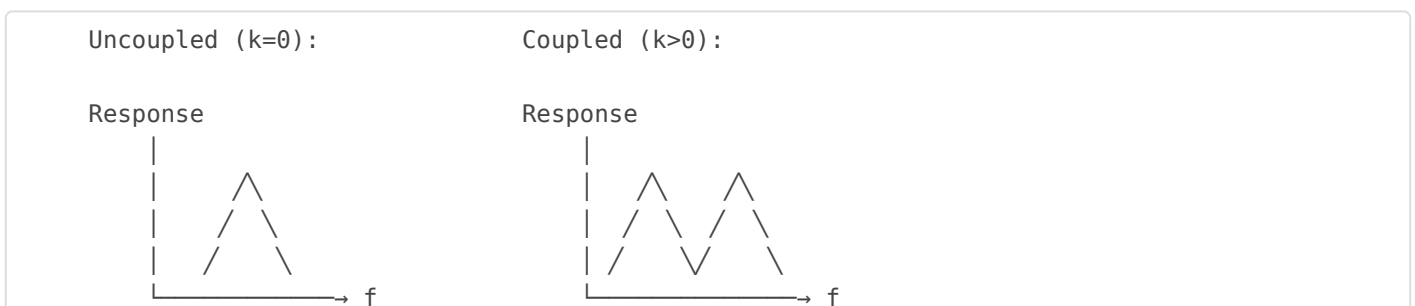Coupled resonators exhibit "mode splitting"—two distinct resonant frequencies instead of one:



f_0 f_1 f_2

Single resonance

Split into two modes

Mode Splitting (equal resonators):

When $f_{0,pri} = f_{0,sec} = f_0$:

$f_{\pm} = f_0 / \sqrt{1 \pm k}$ (lower mode)

$f_{\pm} = f_0 / \sqrt{1 \mp k}$ (upper mode)

Separation increases with coupling coefficient k .

Energy Transfer

Coupling provides a path for energy transfer between primary and secondary:

Coupling	Energy Transfer	VIC Behavior
$k = 0$ (none)	Only through shared current path	Independent resonances
$k = 0.1-0.3$	Moderate magnetic coupling	Slight interaction
$k = 0.5-0.8$	Strong coupling	Significant mode splitting
$k > 0.9$	Very tight coupling	Behaves more like transformer

Bifilar Winding Coupling

Bifilar chokes have inherently high coupling ($k \approx 0.95-0.99$):

Effects of Bifilar Coupling:

- Large mode splitting
- Efficient energy transfer between windings
- Built-in inter-winding capacitance
- Lower overall SRF due to capacitance

Measuring Bifilar Coupling:

1. Measure $L_{\text{series-aid}}$ (windings in series, same polarity)
2. Measure $L_{\text{series-opp}}$ (windings in series, opposite polarity)
3. Calculate: $M = (L_{\text{series-aid}} - L_{\text{series-opp}}) / 4$
4. Calculate: $k = M / \sqrt{L_1 \times L_2}$

Stray Coupling

Even separate chokes may have unintended coupling if placed close together:

Configuration	Typical k	Mitigation
Toroids touching	0.01-0.05	Separate by $>2\times$ diameter
Air-core coils aligned	0.1-0.3	Orient perpendicular
Coils on same rod	0.5-0.9	Use separate cores

Design Considerations

When to Use Coupling:

- Compact design (bifilar combines L1 and L2)
- Intentional transformer action desired
- Specific mode-splitting behavior needed

When to Avoid Coupling:

- Independent tuning of primary and secondary needed
- Simpler analysis desired
- Want predictable single-resonance behavior

Layout Guidelines:

- Toroidal cores have low external field—good for isolation
- Orient coils perpendicular to minimize stray coupling
- Use shielding if isolation is critical
- Measure actual coupling to verify assumptions

Analyzing Coupled VIC Circuits

Coupled Circuit Analysis Steps:

1. Measure or estimate coupling coefficient k
2. Convert to T-equivalent model
3. Analyze as three-inductor circuit
4. Or use simulation with mutual inductance

Simulation Tip: When $k > 0.1$, coupled effects become significant. Always include coupling in simulation if windings share a core or are in close proximity.

VIC Matrix Calculator: The Choke Design module includes coupling coefficient input for bifilar windings. The simulation accounts for mutual inductance effects when analyzing coupled systems.

Next: Energy Efficiency Analysis →

Energy Efficiency

Energy Efficiency Analysis

Understanding energy flow in VIC circuits helps optimize performance and evaluate system efficiency. This page covers how to analyze energy storage, transfer, and dissipation in resonant VIC systems.

Energy in Resonant Circuits

In an LC resonant circuit, energy oscillates between the inductor and capacitor:

Energy Storage:

$$E_L = \frac{1}{2}LI^2 \text{ (energy in inductor)}$$

$$E_C = \frac{1}{2}CV^2 \text{ (energy in capacitor)}$$


At Resonance:


$$E_{\text{total}} = E_{L,\text{max}} = E_{C,\text{max}} = \frac{1}{2}CV_{\text{peak}}^2$$

Peak Energy (example):

- $C = 10 \text{ nF}$, $V_{\text{peak}} = 1000 \text{ V}$
- $E = \frac{1}{2} \times 10 \times 10^{-9} \times 1000^2 = 5 \text{ mJ}$

Energy Flow Diagram

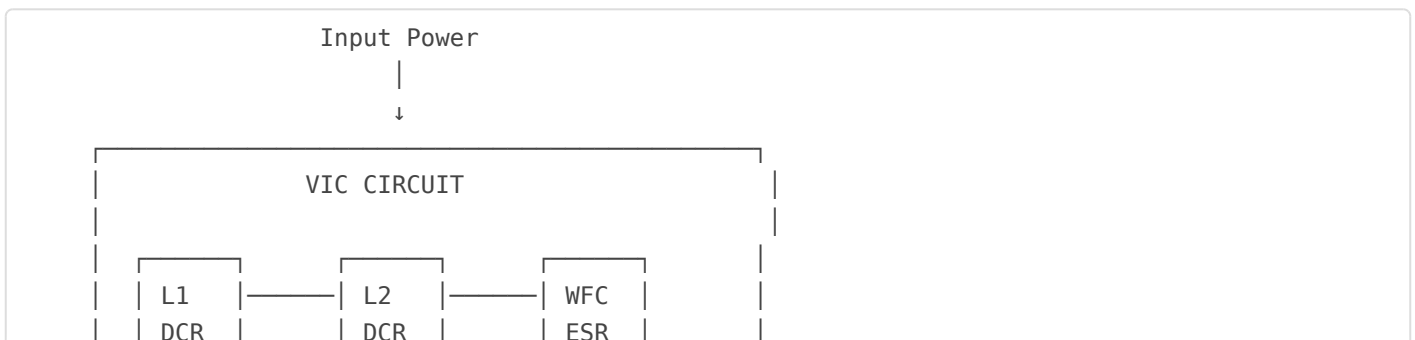

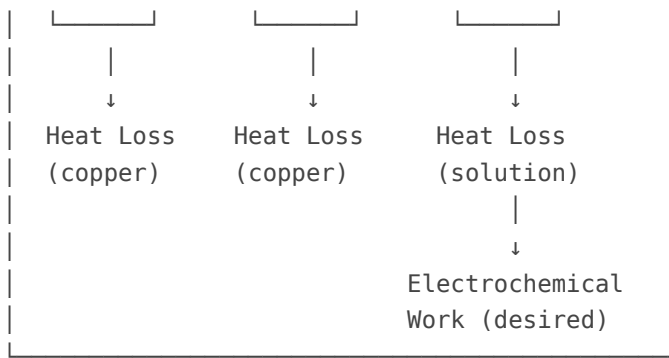

Loss Mechanisms

Loss Type	Formula	How to Minimize
Choke DCR Loss	$P = I^2 R_{DCR}$	Use larger wire, copper
Solution Resistance	$P = I^2 R_{sol}$	Optimize water conductivity
Core Loss	$P \propto f^\alpha \times B^\beta$	Choose low-loss core material
Skin Effect Loss	Increases R at high f	Use Litz wire at high f
Dielectric Loss	$P = \omega C V^2 \times \tan(\delta)$	Use low-loss capacitors

Q Factor and Efficiency

Q factor is directly related to energy efficiency per cycle:

Energy Loss Per Cycle:

$$E_{\text{cycle}} = 2\pi \times E_{\text{stored}} / Q$$

Interpretation:

- Q = 10: Lose 63% of energy per cycle
- Q = 50: Lose 13% of energy per cycle
- Q = 100: Lose 6% of energy per cycle

- $Q = 200$: Lose 3% of energy per cycle

Energy Retention:

After n cycles: $E(n) = E_0 \times e^{(-2\pi n/Q)}$

Power Flow Analysis

Input Power

$$P_{in} = V_{in} \times I_{in} \times \cos(\phi)$$

For pulsed operation:

$$P_{avg} = (1/T) \times \int V(t)I(t)dt$$

Dissipated Power

$$P_{diss} = I_{rms}^2 \times R_{total}$$

Where $R_{total} = R_{DCR1} + R_{DCR2} + R_{sol} + R_{other}$

Useful Power

Power available for electrochemical work:

$$P_{useful} = P_{in} - P_{diss}$$

Or, for the WFC specifically:

$$P_{wfc} = V_{wfc} \times I_{wfc} \times \cos(\phi_{wfc})$$

Efficiency Calculations

Efficiency Type	Formula	Typical Values
Resonant Tank η	$\eta = Q/(Q+1) \approx 1 - 1/Q$	90-99% for high Q

Efficiency Type	Formula	Typical Values
Power Transfer η	$\eta = P_{wfc}/P_{in}$	50-90%
Voltage Multiplication η	V_{out}/V_{in} (at resonance)	10-100x typical

Energy Balance Verification

To verify your analysis is correct, energy must balance:

Steady State:

$$P_{in} = P_{DCR1} + P_{DCR2} + P_{sol} + P_{core} + P_{other}$$

Check:

- Sum all loss mechanisms
- Compare to measured input power
- Large discrepancy indicates missing loss or measurement error

Loss Breakdown Example

Component	Resistance	Power Loss (at 1A)	% of Total
L1 DCR	2.5 Ω	2.5 W	25%
L2 DCR	3.0 Ω	3.0 W	30%
$R_{solution}$	4.0 Ω	4.0 W	40%
Other (core, leads)	0.5 Ω	0.5 W	5%
Total	10 Ω	10 W	100%

Improving Efficiency

High-Impact Improvements:

1. **Reduce largest loss first:** In example above, R_{sol} is 40%—optimize water conductivity
2. **Use larger wire:** Each AWG step down reduces DCR by ~25%
3. **Choose better core:** Low-loss ferrite vs. iron powder
4. **Optimize water conductivity:** Not too high (electrolysis), not too low (resistance loss)
5. **Reduce connection resistance:** Good solder joints, clean contacts

Diminishing Returns:

Once a loss mechanism is <10% of total, further improvement has limited benefit. Focus on the dominant losses.

Thermal Considerations

All dissipated power becomes heat:

Component	Heat Concern	Mitigation
Choke windings	Wire insulation damage	Adequate wire size, ventilation
Ferrite core	Curie temp, permeability change	Keep below rated temperature
Water/WFC	Boiling, capacitance drift	Monitor temperature, allow cooling
Capacitors	ESR heating, life reduction	Use low-ESR types, derate

VIC Matrix Calculator: The simulation module calculates expected power dissipation in each component. Use this to identify thermal hotspots and verify your design won't overheat during operation.

Next: Experimental Validation Methods →

Experimental Validation

Experimental Validation Methods

Theoretical calculations and simulations must be validated with actual measurements. This page covers practical techniques for measuring VIC circuit parameters and comparing results to predictions.

Essential Test Equipment

Equipment	Purpose	Key Specifications
Oscilloscope	Waveform viewing, frequency measurement	2+ channels, 100+ MHz bandwidth
Function Generator	Provide test signals	1 Hz - 1 MHz, variable duty cycle
LCR Meter	Measure L, C, R	Multiple test frequencies (1 kHz, 10 kHz)
Multimeter	DC resistance, voltage	True RMS, low-ohm capability
Current Probe	Non-contact current measurement	AC/DC, appropriate bandwidth
High-Voltage Probe	Measure high voltages safely	1000:1 or 100:1, rated voltage

Component Verification

Measuring Inductance

Method 1: LCR Meter (Preferred)

1. Set LCR meter to inductance mode
2. Select test frequency (1 kHz typical)
3. Connect inductor, read value
4. Repeat at 10 kHz to check for frequency dependence

Method 2: Resonance with Known C

1. Connect inductor with known capacitor C
2. Drive with function generator, sweep frequency
3. Find resonant frequency f_0 (voltage peak)
4. Calculate: $L = 1/(4\pi^2 f_0^2 C)$

Measuring DCR

Four-Wire (Kelvin) Measurement:

For accurate low-resistance measurement, use 4-wire method to eliminate lead resistance:

- Use dedicated low-ohm meter
- Or use LCR meter in R mode
- Allow reading to stabilize (self-heating)

Expected accuracy: $\pm 1-5\%$ compared to calculated value

Measuring WFC Capacitance

1. Fill WFC with water at operating temperature
2. Measure with LCR meter at 1 kHz and 10 kHz
3. Values should be similar (if EDL effects are small)
4. Note the ESR reading as well

Expected accuracy: $\pm 10\text{-}20\%$ compared to calculated value

Resonant Frequency Measurement

Frequency Sweep Method

Setup:

```
Function → [VIC ] → Oscilloscope
Generator [Circuit] Ch1: Input
                Ch2: Output (across WFC)
```

Procedure:

1. Set function generator to low amplitude sine wave
2. Start at low frequency (1/10 of expected f_0)
3. Slowly increase frequency while watching Ch2 amplitude
4. Note frequency of maximum amplitude—this is f_0
5. Also note -3dB frequencies (where amplitude = $0.707 \times$ peak)

Calculate Q from Measurement:

$$Q = f_0 / (f_{\text{high}} - f_{\text{low}}) = f_0 / \text{BW}$$

Phase Measurement Method

1. Display both input current and output voltage
2. Use X-Y mode or measure phase with oscilloscope
3. At resonance, phase difference = 0°
4. More accurate than amplitude peak for high-Q circuits

Q Factor Measurement

Method 1: Bandwidth

Measure -3dB bandwidth and calculate:

$$Q = f_0 / BW$$

Method 2: Ring-Down

1. Excite circuit with single pulse at f_0
2. Observe decaying oscillation on oscilloscope
3. Count cycles to decay to $1/e$ (37%)
4. $Q \approx \pi \times$ (number of cycles to $1/e$ decay)

Alternatively, measure time constant τ :

$$\tau = 2L/R = Q / (\pi f_0)$$

Method 3: Voltage Magnification

1. Measure input voltage V_{in}
2. Measure output voltage V_{out} at resonance
3. $Q \approx V_{out}/V_{in}$

Caution: This assumes lossless input coupling. Actual Q may be higher due to source impedance effects.

Comparing Calculated vs. Measured

Parameter	Acceptable Difference	If Larger Difference
Inductance	$\pm 20\%$	Check core μ_r , turn count
DCR	$\pm 10\%$	Check wire gauge, connections
WFC Capacitance	$\pm 20\%$	Check geometry, water level
Resonant Frequency	$\pm 15\%$	Check L and C values
Q Factor	$\pm 30\%$	Look for missing losses

Troubleshooting Discrepancies

Measured f? Lower than Calculated:

- Stray capacitance adding to total C
- Actual L higher than calculated
- Check for loose connections (add L)

Measured f? Higher than Calculated:

- Actual L lower (core saturation, wrong μ_r)
- WFC capacitance overestimated
- Air bubbles reducing effective C

Measured Q Lower than Calculated:

- Additional losses not accounted for
- Core losses at operating frequency
- Poor connections adding resistance
- Radiation losses at high frequency

No Clear Resonance Observed:

- Operating above SRF (choke is capacitive)
- Very low Q ($Q < 2$) makes resonance hard to see
- Measurement setup loading the circuit

Documentation Template

Record for Each Test:

Date: _____

Circuit ID: _____

COMPONENT VALUES (Calculated / Measured):

L1: _____ mH / _____ mH
L2: _____ mH / _____ mH
DCR1: _____ Ω / _____ Ω
DCR2: _____ Ω / _____ Ω
C_wfc: _____ nF / _____ nF
C1: _____ nF / _____ nF

RESONANCE (Calculated / Measured):
f_o_primary: _____ kHz / _____ kHz
f_o_secondary: _____ kHz / _____ kHz

PERFORMANCE (Calculated / Measured):
Q: _____ / _____
Bandwidth: _____ Hz / _____ Hz
V_magnification: _____ / _____

NOTES:

Safety Considerations

?? High Voltage Warning:

- VIC circuits can develop high voltages at resonance
- Always use proper high-voltage probes
- Keep one hand in pocket when probing live circuits
- Discharge capacitors before handling

?? Gas Production:

- WFC produces hydrogen and oxygen—ensure ventilation
- No open flames or sparks near operating cell
- Use appropriate gas collection if needed

Best Practice: Always compare measured values to calculator predictions. This builds confidence in both your construction skills and the calculator's accuracy. Document discrepancies—they often

reveal important lessons about real-world effects.

Chapter 8 Complete. See Appendices for reference tables and formulas. →

Understanding Resonant Action in the Water Fuel Cell

This article explains the principle of **Resonant Action** — the mechanism by which Stan Meyer's Water Fuel Cell achieves water dissociation through matched mechanical and electrical resonance, rather than brute-force electrolysis. We walk through the physics, the patent language, and the math to arrive at a complete, actionable design chain.

Why Water's Dielectric Properties Matter

The Voltage Intensifier Circuit (VIC) operates in the **1 kHz - 100 kHz range**, where both dipolar and ionic mechanisms in water are fully active. At these frequencies, water's dielectric constant remains very high (~78-80), making it an excellent capacitor dielectric inside the gas processor tubes.

The dipolar relaxation cutoff for water doesn't occur until **~17-20 GHz** — far above VIC operating range. This means at our target frequencies, water molecules can physically respond to the applied electric field. This is the basis of Stan's **Electrical Polarization Process (EPP)**.

Patents **#5,149,407** and **WO8912704A1** describe this explicitly:

“Water molecules are broken down into hydrogen and oxygen gas atoms in a capacitive cell by a polarization and resonance process **dependent upon the dielectric properties of water.**”

Complex Permittivity

Water's permittivity has two components that matter for VIC design:

- **Real part (ϵ')** — determines the cell's capacitance and therefore your resonant frequency
- **Imaginary part (ϵ'')** — the loss tangent, which directly reduces your circuit's Q factor

Because permittivity changes with temperature, conductivity, and frequency, your water "capacitor" is a moving target. This is why VIC tuning can drift during operation, and why **water**

purity matters — too many dissolved ions dump current into conductance instead of polarization.

The Ionization-Conductivity Feedback Loop

Applying voltage to water creates a chain reaction:

1. Voltage **ionizes** the molecule → creates H^+ and OH^- carriers
2. **Conductivity goes up** → loss tangent (ϵ'') rises → **Q factor drops**
3. Resonance degrades

This is precisely why the VIC uses **pulsed voltage** rather than continuous DC. Hit the molecule hard and fast, then let it rest. The rest period allows electrical polarization to weaken the covalent bond *before* excessive ionization destroys the resonant condition.

Apply continuous voltage and conductivity keeps climbing — the cell stops acting like a capacitor and starts acting like a resistor. You've built an expensive water heater, not a fuel cell.

Per Patent **#4,936,961**, the key is that electrical polarization weakens the covalent bond *before* full ionization occurs. The WFC operates in the narrow window between polarization and brute-force electrolysis.

Corrugated Geometry: Momentary Entrapment

Corrugated cell surfaces serve a dual purpose that goes beyond simple surface area increase:

- **Peak of corrugation** → intense local electric field → strong EPP → bonds weakened at focal points
- **Bulk water between peaks** → lower average field → lower ionization → conductivity stays manageable

This gives you *localized* electrical polarization without destroying the Q factor in the bulk medium. You can run higher effective field gradients than smooth tubes at the same voltage, before conductivity kills your resonance.

Patent EP0103656A2 — Resonant Cavity for Hydrogen Generator

Filed December 14, 1982, this is one of Stan's earliest European filings. The patent text on the corrugated exciter (Figure 6) is explicit about *why* corrugations matter:

“ "Instead of a forward direct line back-and-forth path of the atom flow, the corrugations of the convex 47 and concave 49 surfaces causes the atoms to move in forward and backward / back-and-forth path."

“ "The increased surface area provided by the corrugations and creating the resonant cavity, thus enhances the sub-atomic action."

The corrugations aren't just field concentrators — they force molecules into an oscillatory path, increasing **residence time** in the high-gradient zone. This is **Momentary Entrapment to assist Resonant Action**: the geometry traps the molecule long enough for multiple resonant cycles to act on it, rather than letting it blow straight through the gap in a single cycle.

A water molecule at room temperature moves at roughly **600 m/s** thermally. In a 1 cm gap, it transits in about 16 microseconds — barely one cycle at 60 kHz. The corrugation multiplies the effective interaction time by 5-10x, turning a single glancing pass into meaningful resonant coupling.

The Key Insight: Cavity Spacing = Wavelength

The critical passage comes from Patent **#4,798,661** (Gas Generator Voltage Control Circuit):

“ "The phenomena that the spacing between two objects is related to the wavelength of a physical motion between the two objects is utilized herein."

"The pulsing voltage on the plate exciters applying a physical force is matched in repetition rate to the wavelength of the spacing of the plate exciters. The physical motion of the hydrogen and oxygen charged atoms being attracted to the opposite polarity zones will go into resonance. The self sustaining resonant motion of the hydrogen and oxygen atoms of the water molecule greatly enhances their disassociation from the water molecule."

The plate spacing is **not arbitrary**. It *is* the wavelength. Charged ions get attracted across the gap, overshoot, get pulled back, overshoot again. When the spacing matches the wavelength of that motion at the pulse frequency, they enter **self-sustaining resonance**.

The governing relationship:

$$\text{spacing} = \text{drift velocity} / \text{pulse frequency}$$

The drift velocity here is **not** the thermal velocity (~600 m/s) — it's the velocity of charged ions under the applied electric field. This is controllable, and it's how you tune the system.

Calculating Resonant Action for a 1/16" Gap

Using $F = ma$ and the cavity spacing relationship, we can calculate the force and frequency needed for Stan's standard 1/16" tube gap:

Parameter	Value
Gap	1/16" = 1.587 mm
λ (spacing)	0.001587 m
$f = v / \lambda$	600 / 0.001587 = ~378 kHz
$m(\text{H}_2\text{O})$	2.99×10^{-26} kg
Amplitude (gap/2)	0.794 mm
$\omega = 2\pi f$	2.376×10^6 rad/s
$F = m \cdot A \cdot \omega^2$	$\sim 1.34 \times 10^{-16}$ N per molecule
$E = F / q$	~ 838 V/m
$V = E \times d$	~1.3 volts to sustain resonance

The sustaining voltage appears tiny — and that's the point. You don't need kilovolts to *sustain* resonance. You need kilovolts to **overcome damping, collisions, and initiate resonance in**

the first place. Once the molecule is oscillating resonantly, minimal energy maintains it.

Dual Resonance: The Unified System

This is the insight that ties everything together. There are **two resonances** that must be matched:

1. **Physical (mechanical) resonance:** the water molecule bouncing across the gap at 378 kHz
2. **Electrical resonance:** the VIC's LC tank circuit ringing at 378 kHz

When both are matched, maximum energy couples into the molecule at peak vulnerability.

Calculating the Choke Inductance

If mechanical resonance = 378 kHz and water cell capacitance \approx 800 pF (typical for a 3" concentric tube cell), then:

$$f = 1 / (2\pi\sqrt{LC})$$

Solving for L:

$$L = 1 / ((2\pi f)^2 \times C)$$

$$L = 1 / ((2\pi \times 378,000)^2 \times 800 \times 10^{-12})$$

$$L \approx 221 \mu\text{H}$$

This is notably lower than the 500 μH - 2 mH values seen in most replication attempts. The reason: most builders tune to 40-70 kHz without matching the physical gap. **Change the gap, you change everything.**

The Dual Voltage Waveform

Stan's patent language from #4,798,661 describes the waveform strategy:

“The pulsating d.c. voltage and the duty cycle pulses have a maximum amplitude of the level that would cause electron leakage. Varying of the amplitude to an amplitude of maximum level to an amplitude below the maximum level of the pulses, provide an average amplitude below the maximum limit; but with the force of the maximum limit.”

This is achieved with **two variacs (0-120V each)** and a **flip-flop switching circuit**:

- **Peak voltage (Va)**: Hits the electron leakage threshold — maximum force. This kicks the molecule into oscillation at the resonant frequency. Think of it like striking a tuning fork.
- **Low voltage (Vb)**: The duty cycle sustain level. Keeps the molecule oscillating without crossing into electron leakage territory. Like keeping a pendulum swinging with just enough push.

The flip-flop switches between these two voltage levels at the resonant frequency. You're not pulsing ON/OFF — you're pulsing between **two precise voltage levels**. The peak delivers maximum force while the duty cycle keeps average energy below the leakage threshold.

Finding Your Electron Leakage Threshold

As you increase the peak variac setting, watch for these indicators:

- Gas production climbs while current stays low — you're in the **polarization regime**
- Current draw suddenly climbs faster than gas production — you've crossed into **electrolysis**
- Water temperature begins rising (ohmic heating)
- A sharp "knee" appears on your ammeter curve

Back off just below that knee — that's your Va max. Lock it in, then use the second variac to set the lower sustain level.

The Complete Design Chain

Every parameter in the WFC connects to every other parameter. It is one unified system:

```
Gap spacing (1/16" = 1.587 mm)
  → Molecular resonant frequency (378 kHz)
    → Choke inductance (221 µH for 800 pF cell)
      → Drive frequency matches mechanical + electrical resonance
        → Peak voltage set at electron leakage threshold
          → Dual-variatic waveform: peak force + duty cycle sustain
            → Molecular resonance driving (NOT electrolysis)
```

Most replication attempts treat these as separate problems — picking a gap, picking a frequency, winding a choke to whatever value, and hoping it works. The design chain above shows they are all interdependent. Start with your gap, derive everything else.

Volt-Seconds & Transformer Design

When designing the step-up transformer for the VIC, the core saturation limit is governed by volt-seconds:

$$B_{\text{peak}} = (V_{\text{in}} \times t_{\text{on}}) / (N_{\text{primary}} \times A_{\text{e}})$$

$$N_{\text{min}} = (V_{\text{in}} \times t_{\text{on}}) / (B_{\text{sat}} \times A_{\text{e}})$$

A common question is whether turns ratio alone matters. It doesn't — 5:1, 50:10, and 500:100 are **not the same design**, even though the ratio is identical:

Configuration	Characteristics
5 : 1	Low inductance, requires higher frequency (100 kHz+), tight winding, low copper loss
50 : 10	10× primary inductance, handles lower frequencies, more copper, more inter-winding capacitance
500 : 100	Large core required, parasitic capacitance degrades pulse edges

The key relationships:

- **Higher frequency** = shorter t_{on} = fewer volt-seconds per cycle = fewer turns needed
- **More turns** = less flux per turn = lower frequency operation on the same core
- **Optimum** = where copper loss and core loss curves intersect

Patents Referenced

Patent	Title	Relevance
US #4,936,961	Method for Production of Fuel Gas	Primary VIC patent; EPP mechanism
US #4,798,661	Gas Generator Voltage Control Circuit	Cavity spacing = wavelength; dual voltage waveform
US #5,149,407	Process & Apparatus for Production of Fuel Gas	Polarization dependent on dielectric properties
EP0103656A2	Resonant Cavity for Hydrogen Generator	Corrugated exciter geometry (1982)
WO8912704A1	Process & Apparatus for Production of Fuel Gas	World patent; dielectric-dependent dissociation
Serial 06/367,052	Earlier corrugated surface exciter	Referenced as prior design in EP0103656A2