

VIC Circuit Theory

- [VIC Introduction](#)
- [Primary Side](#)
- [Secondary Side](#)
- [Resonant Charging](#)
- [Step Charging](#)

VIC Introduction

What is a VIC Circuit?


The Voltage Intensifier Circuit (VIC) is a resonant circuit topology designed to develop high voltages across a water fuel cell (WFC) while drawing relatively low current from the source. Originally conceived by Stanley Meyer, the VIC uses the principles of resonance and voltage magnification to create conditions favorable for water dissociation.

The Basic Concept

At its core, the VIC is a series resonant circuit that uses inductors (chokes) and capacitors to magnify voltage. Unlike conventional electrolysis that uses brute-force DC current, the VIC aims to:

- **Maximize voltage** across the water fuel cell
- **Minimize current** draw from the power source
- **Use resonance** to achieve efficient energy transfer
- **Exploit the capacitive nature** of the water cell

The VIC Block Diagram

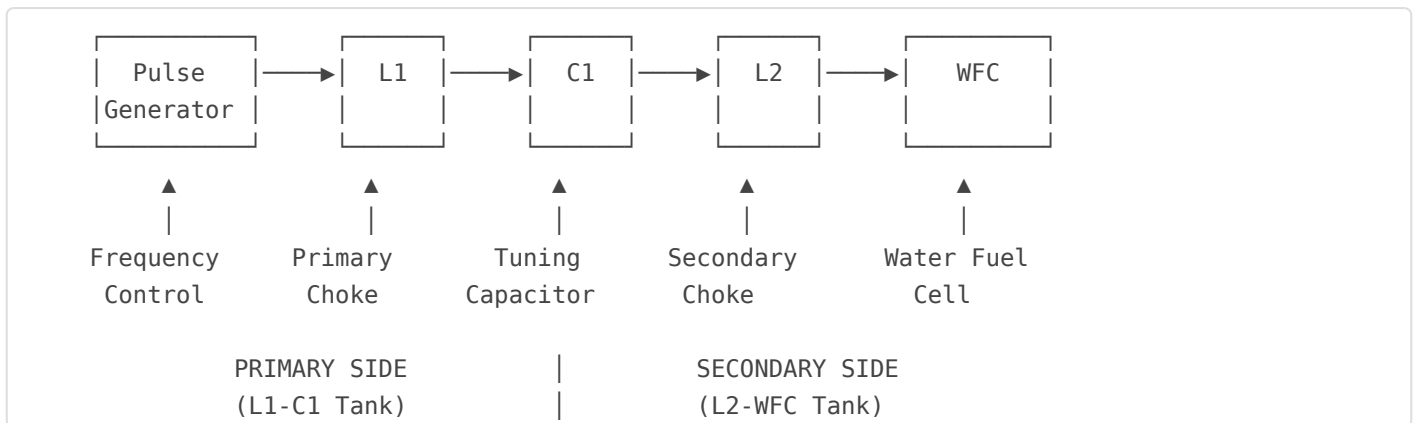

Key Components

Component	Symbol	Function
-----------	--------	----------

Pulse Generator	—	Provides driving signal at resonant frequency
Primary Choke	L1	Current limiting, energy storage, voltage magnification
Tuning Capacitor	C1	Sets primary resonant frequency with L1
Secondary Choke	L2	Further voltage magnification, resonance with WFC
Water Fuel Cell	WFC	Capacitive load where water dissociation occurs

Operating Principle

Step 1: Pulse Excitation

The pulse generator provides a square wave or pulsed DC signal at or near the resonant frequency of the primary tank circuit (L1-C1).

Step 2: Primary Resonance

The L1-C1 combination resonates, building up voltage across C1 that can be many times the input voltage (determined by Q factor).

Step 3: Energy Transfer

The amplified voltage drives current through L2, which further builds up energy and transfers it to the WFC.

Step 4: Secondary Resonance

If L2 and WFC are tuned together, a second stage of voltage magnification occurs, creating very high voltages across the water.

Step 5: Water Interaction

The high voltage across the WFC creates a strong electric field in the water, affecting the molecular bonds of H₂O.

The "Matrix" Concept

The term "VIC Matrix" refers to the interconnected relationship between all circuit parameters. Everything is connected:

- Changing L1 affects the primary resonant frequency
- The resonant frequency must match the pulse generator
- L2 and WFC capacitance determine secondary resonance
- All inductances and capacitances are linked through the desired frequency
- The Q factors determine voltage magnification at each stage

This is why the VIC Matrix Calculator exists—to help navigate these complex interdependencies.

Circuit Variations

Basic VIC (Two-Choke)

Uses separate L1 and L2 chokes with discrete C1 and WFC capacitance.

Transformer-Coupled VIC

L1 and L2 are wound on the same core, creating transformer action between primary and secondary.

Bifilar VIC

Uses bifilar-wound chokes where two windings are wound together, creating inherent capacitance and magnetic coupling.

Single-Choke VIC

Simplified version where one choke resonates directly with the WFC capacitance.

What Makes VIC Different from Electrolysis?

Parameter	Conventional Electrolysis	VIC Approach
Power Type	DC (constant current)	Pulsed/AC (resonant)

Parameter	Conventional Electrolysis	VIC Approach
Voltage	1.5-3V (above decomposition)	Hundreds to thousands of volts
Current	High (amps)	Low (milliamps)
Frequency	0 Hz (DC)	kHz to MHz range
WFC View	Resistive load	Capacitive load
Energy Mechanism	Electron transfer	Electric field stress

Goals of VIC Design

1. **Maximize Q factor:** Higher Q = more voltage magnification
2. **Achieve resonance:** All components tuned to operating frequency
3. **Match impedances:** Efficient energy transfer between stages
4. **Maintain stability:** Prevent frequency drift and oscillation problems
5. **Deliver energy to WFC:** Create conditions for water molecule stress

Key Insight: The VIC treats water not as a resistive medium to push current through, but as a dielectric capacitor to be charged with high voltage. This fundamental difference drives all aspects of VIC design and is why traditional electrolysis equations don't apply.

Next: Primary Side (L1-C1) Analysis →

Primary Side


Primary Side (L1-C1) Analysis

The primary side of the VIC consists of the first inductor (L1) and tuning capacitor (C1). This stage receives the driving signal and provides the first stage of voltage magnification. Understanding its behavior is crucial for successful VIC design.

Primary Tank Circuit

L1 and C1 form a series resonant tank circuit. At the resonant frequency, this circuit:

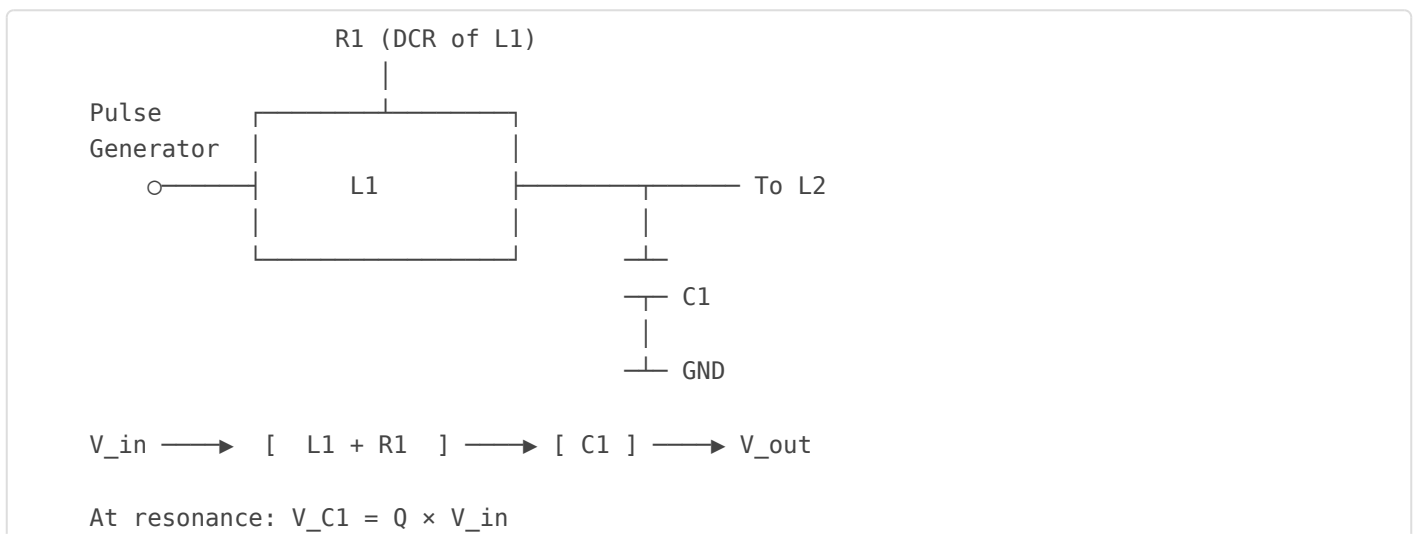- Has minimum impedance (ideally just the DC resistance)
- Draws maximum current from the source
- Develops magnified voltage across L1 and C1



Resonant Frequency Calculation

Primary Resonant Frequency:

$$f_r = \frac{1}{2\pi\sqrt{L1 \times C1}}$$

Rearranging to Find Components:

$$L1 = \frac{1}{4\pi^2 f_r^2 C1}$$

$$C1 = 1 / (4\pi^2 f^2 L1)$$

Example Calculations

Target f_0	Given L1	Required C1
10 kHz	1 mH	253 nF
10 kHz	10 mH	25.3 nF
25 kHz	1 mH	40.5 nF
50 kHz	500 μ H	20.3 nF

Q Factor of Primary Side

The Q factor determines voltage magnification:

Q Factor:

$$Q_{L1C} = (2\pi \times f \times L1) / R1 = X_{L1} / R1$$

Voltage Magnification:

$$V_{C1} = Q_{L1C} \times V_{in}$$

Example:

- $f_0 = 10 \text{ kHz}$, $L1 = 10 \text{ mH}$, $R1 = 10 \Omega$
- $X_{L1} = 2\pi \times 10,000 \times 0.01 = 628 \Omega$
- $Q = 628 / 10 = 62.8$
- With 12V input: $V_{C1} = 62.8 \times 12 = 754V$

Characteristic Impedance

The characteristic impedance of the primary tank affects matching:

$$Z_0 = \sqrt{L1 / C1}$$

Relationship to Q:

$$Q = Z_0 / R_1$$

Higher Z_0 (more L, less C) means higher Q for same resistance.

Design Trade-offs

Design Choice	Advantages	Disadvantages
High L1, Low C1	Higher Z_0 , potentially higher Q	More wire, higher DCR, harder to wind
Low L1, High C1	Less wire, lower DCR, easier construction	Lower Z_0 , may need larger capacitor
High frequency	Smaller components, lower SRF concern	Skin effect losses, harder switching
Low frequency	Lower losses, easier switching	Larger components, SRF may be issue

Current and Power Considerations

At resonance, the circuit draws maximum current:

Resonant Current:

$$I_{res} = V_{in} / R_1$$

Power from Source:

$$P_{in} = V_{in}^2 / R_1 = I_{res}^2 \times R_1$$

Reactive Power (circulating):

$$P_{reactive} = V_{C1} \times I_{res} = Q \times P_{in}$$

Note: The reactive power circulates between L1 and C1 but is not consumed.

Bandwidth and Tuning Sensitivity

The 3dB bandwidth of the primary tank:

$$BW = f_0 / Q_{L1C}$$

Example:

$$f_0 = 10 \text{ kHz}, Q = 50 \rightarrow BW = 200 \text{ Hz}$$

The driving frequency must be within ± 100 Hz of f_0 for good response.

Practical Implication:

High-Q circuits are sensitive to component tolerances and temperature drift. You may need PLL (Phase-Locked Loop) control to maintain resonance.

Component Selection Guidelines

L1 (Primary Choke)

- **Inductance:** 100 μ H to 100 mH typical
- **DCR:** As low as practical (determines Q)
- **SRF:** Should be well above operating frequency (10 \times minimum)
- **Core:** Ferrite, iron powder, or air-core depending on frequency
- **Wire:** Copper preferred; resistance wire reduces Q

C1 (Tuning Capacitor)

- **Value:** Selected to resonate with L1 at desired frequency
- **Voltage rating:** Must exceed $Q \times V_{in}$
- **Type:** Film (polypropylene, polyester) or ceramic
- **ESR:** Low ESR for minimal losses
- **Temperature stability:** NPO/C0G ceramic or film preferred

Practical Assembly Tips

1. **Measure L1 accurately:** Use an LCR meter at multiple frequencies
2. **Start with calculated C1:** Then fine-tune for best response
3. **Use variable capacitor or parallel caps:** For easy tuning
4. **Check for SRF:** Ensure L1's SRF is well above f_0
5. **Monitor temperature:** Component values drift with heat

VIC Matrix Calculator: The calculator determines optimal L1 and C1 values based on your target frequency and available components. It also shows the expected Q factor and voltage magnification.

Next: Secondary Side (L2-WFC) Analysis →


Secondary Side

Secondary Side (L2-WFC) Analysis

The secondary side of the VIC consists of the second inductor (L2) and the water fuel cell (WFC) acting as a capacitor. This stage receives the amplified signal from the primary and delivers the final voltage to the water. Proper design of this stage is critical for efficient energy transfer to the WFC.

Secondary Tank Circuit

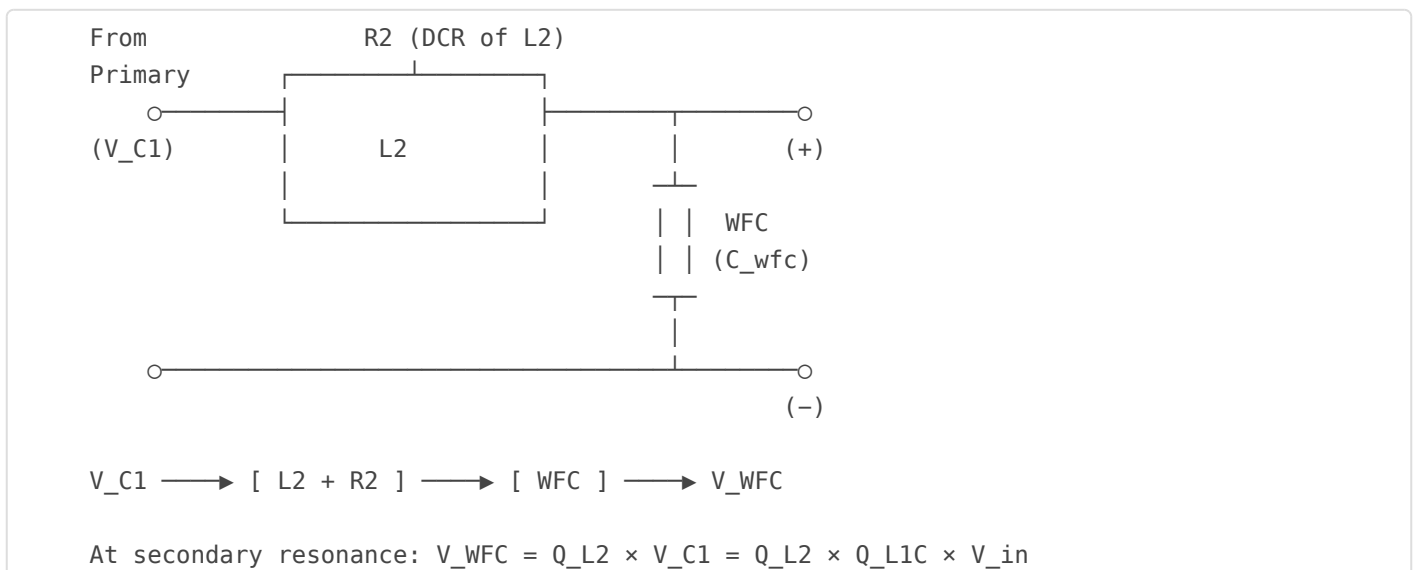L2 and the WFC capacitance form the secondary resonant tank:



The WFC as a Capacitor

The water fuel cell presents a complex impedance, but at VIC frequencies, it behaves predominantly as a capacitor:

WFC Capacitance Components:

- **Geometric capacitance:** $C_{\text{geo}} = \epsilon_0 \epsilon_r A/d$
- **EDL capacitance:** C_{edl} (in series, at each electrode)
- **Effective capacitance:** $C_{\text{wfc}} = f(C_{\text{geo}}, C_{\text{edl}}, \text{frequency})$

At typical VIC frequencies (1-50 kHz), C_{wfc} is dominated by C_{geo} .

Secondary Resonant Frequency

Secondary Resonance:

$$f_{\text{secondary}} = 1 / (2\pi \sqrt{L_2 \times C_{\text{wfc}}})$$

For Maximum Voltage Transfer:

$$\text{Ideally, } f_{0\text{secondary}} = f_{0\text{primary}}$$

$$\text{This means: } L_1 \times C_1 = L_2 \times C_{\text{wfc}}$$

Q Factor of Secondary Side

The secondary Q factor determines the second stage of voltage magnification:

Secondary Q Factor:

$$Q_{L_2} = (2\pi \times f \times L_2) / (R_2 + R_{\text{wfc}})$$

Where R_{wfc} is the effective resistance of the WFC (solution resistance + losses).

Total Voltage Magnification:

$$V_{\text{WFC}} = Q_{L_1 C} \times Q_{L_2} \times V_{\text{in}}$$

Example:

- $Q_{L1C} = 30, Q_{L2} = 20, V_{in} = 12V$
- $V_{WFC} = 30 \times 20 \times 12 = 7,200V$ theoretical

Cascaded Resonance Effects

When both stages resonate at the same frequency, the effects multiply:

Configuration	Total Magnification	Notes
Only primary resonance	Q_{L1C}	L2-WFC not tuned
Only secondary resonance	Q_{L2}	L1-C1 not tuned
Dual resonance	$Q_{L1C} \times Q_{L2}$	Maximum magnification
Harmonic secondary	Variable	Secondary at $2f_0, 3f_0$, etc.

Impedance Matching Considerations

For efficient energy transfer between primary and secondary:

Characteristic Impedance Match:

$$Z_{\text{primary}} = \sqrt{L1/C1}$$

$$Z_{\text{secondary}} = \sqrt{L2/C_{wfc}}$$

Matching these impedances can improve energy transfer, though it's not always achievable or necessary.

Effect of WFC Properties on Secondary

WFC Parameter	Effect on Secondary	Design Response
Higher C_{wfc}	Lower f_0 , lower Z_0	Increase L2 or reduce C1
Higher R_{wfc}	Lower Q_{L2}	Use purer water or optimize gap

WFC Parameter	Effect on Secondary	Design Response
Larger electrode area	Higher C_{wfc}	Requires larger L2
Narrower gap	Higher C_{wfc} , lower R_{wfc}	Trade-off between C and R

Bifilar Choke Considerations

When L2 is bifilar wound (or when L1 and L2 are wound together as a bifilar pair):

- **Inherent capacitance:** The bifilar winding has capacitance between turns
- **Magnetic coupling:** Energy transfers inductively between windings
- **Lower SRF:** The inter-winding capacitance lowers self-resonant frequency
- **Complex tuning:** The system becomes a coupled resonator

Calculating L2 for Given WFC

Given: Target frequency and WFC capacitance

$$L_2 = 1 / (4\pi^2 f^2 C_{wfc})$$

Example:

- $f_0 = 10 \text{ kHz}$
- $C_{wfc} = 5 \text{ nF}$ (typical small WFC)
- $L_2 = 1 / (4\pi^2 \times 10^4 \times 5 \times 10^{-9}) = 50.7 \text{ mH}$

Sanity check: This is a reasonable inductance, achievable with ~500-1000 turns on a ferrite core.

Power Delivery to WFC

The actual power delivered to the WFC depends on its resistive component:

Power in WFC Resistance:

$$P_{wfc} = I_{wfc}^2 \times R_{wfc}$$

Where:

$$I_{wfc} = V_{WFC} / Z_{wfc} \quad V_{WFC} \times ? \times C_{wfc}$$

This power heats the water and drives electrochemical reactions.

Voltage Distribution Across WFC

The high voltage across the WFC creates an electric field:

Electric Field in WFC:

$$E = V_{WFC} / d$$

Where d is the electrode gap.

Example:

- $V_{WFC} = 1000V$, $d = 1mm$
- $E = 1000V / 0.001m = 1 \text{ MV/m} = 10 \text{ kV/cm}$

This is a substantial electric field that can influence molecular behavior in water.

Design Guidelines for L2

1. **Match resonant frequency:** L2 should resonate with C_{wfc} at the same frequency as L1-C1
2. **Minimize DCR:** R2 directly reduces Q_{L2} and thus voltage magnification
3. **Consider coupling:** If using transformer-coupled design, mutual inductance matters
4. **Account for WFC changes:** C_{wfc} varies with temperature, voltage, and bubble formation
5. **Leave tuning margin:** Design L2 slightly higher, fine-tune with small series capacitor if needed

Key Insight: The secondary side is where VIC theory meets reality. The WFC is not an ideal capacitor—it has losses, frequency-dependent behavior, and changes during operation. Successful

VIC design must account for these real-world effects.

Next: Resonant Charging Principle →

Resonant Charging


Resonant Charging Principle

Resonant charging is a technique where energy is transferred to a capacitive load (the WFC) in a controlled, oscillatory manner. Unlike direct DC charging, resonant charging can achieve higher efficiency and allows voltage magnification beyond the source voltage.

Conventional vs. Resonant Charging

Aspect	DC Charging (R-C)	Resonant Charging (L-C)
Final voltage	$= V_{\text{source}}$	Can exceed V_{source} (up to $2\times$ for half-wave)
Energy efficiency	50% max (half lost in R)	Can approach 100% (minimal loss in L)
Charging curve	Exponential (slow)	Sinusoidal (faster)
Peak current	V/R at start	V/Z_0 (controlled by L)

Basic Resonant Charging Circuit

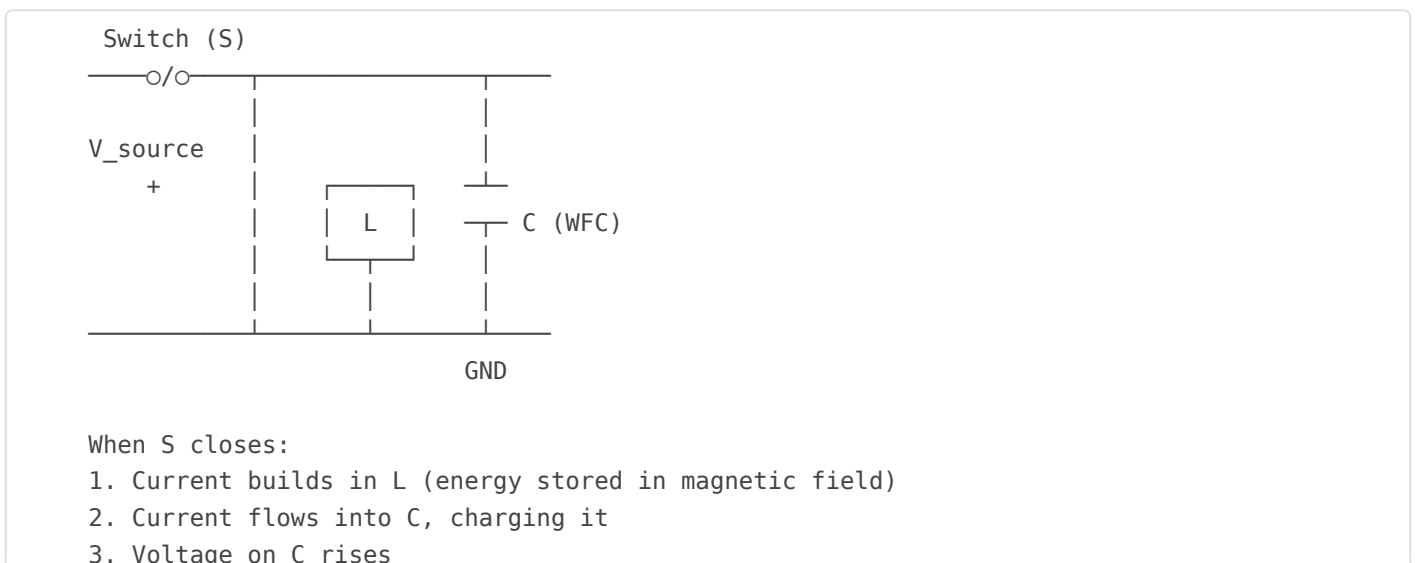

Half-Cycle Resonant Charging

In half-cycle mode, the switch opens when capacitor voltage reaches maximum:

Ideal Half-Cycle Charging (lossless):

$$V_{C,\max} = 2 \times V_{\text{source}}$$

Charging Time:

$$t_{\text{charge}} = \pi(LC) = \pi/\omega = 1/(2f)$$

This is exactly half the resonant period.

Why 2x Voltage?

Energy Conservation:

1. Initially: All energy in source (voltage V_s)
2. Quarter cycle: Energy split between L (current max) and C ($V = V_s$)
3. Half cycle: All energy in C, current = 0
4. For energy to be conserved: $\frac{1}{2}CV_c^2 = C \times V_s^2$ (accounting for work done by source)
5. This gives $V_c = 2V_s$

Resonant Charging with Losses

Real circuits have losses that reduce the voltage gain:

With Resistance (damped case):

$$V_{C,\max} = V_{\text{source}} \times (1 + e^{-R/(2(L/C))})$$

$$V_{C,\max} = V_{\text{source}} \times (1 + e^{-R/(2Q)})$$

Approximation for high Q:

$$V_{C,\max} \approx 2V_{\text{source}} \times (1 - R/(4Q))$$

Voltage Gain vs. Q Factor

Q Factor	$V_{C,max}/V_{source}$	Efficiency
∞ (ideal)	2.00	100%
100	1.98	98.4%
50	1.97	96.9%
20	1.92	92.5%
10	1.85	85.5%
5	1.73	73%

Continuous Resonant Excitation

In the VIC, instead of single pulses, we drive the circuit continuously at the resonant frequency:

Steady-State Resonance:

Energy from the source compensates for losses each cycle, maintaining a steady oscillation amplitude.

Voltage Magnification:

$$V_C = Q \times V_{source}$$

This is much greater than the 2x from single-pulse resonant charging when $Q > 2$.

Resonant Charging in VIC Context

The VIC uses resonant charging principles in several ways:

1. **Primary tank:** C1 is resonantly charged through L1
2. **Secondary transfer:** Energy transfers resonantly to WFC through L2
3. **Cumulative effect:** Multiple stages multiply the magnification

Timing and Switching

For optimal resonant charging:

Critical Timing Points:

- **Turn-on:** When capacitor voltage is minimum (or at desired starting point)
- **Turn-off:** When current through inductor reaches zero (zero-current switching)
- **Period:** Should match or be a harmonic of the resonant frequency

Zero-Current Switching (ZCS):

Turning off when current is zero minimizes switching losses and eliminates inductive kick.

Energy Flow Analysis

Time →



Energy in C: High → Low → High → Low

Energy in L: Low → High → Low → High

Total energy (minus losses) remains constant in steady state.

Advantages of Resonant Charging for WFC

- **High voltage:** Achieves voltages beyond source capability
- **Low current draw:** Source only provides loss compensation
- **Controlled energy delivery:** Sinusoidal rather than impulsive
- **Efficient:** Minimal resistive losses when Q is high
- **Self-limiting:** Voltage limited by Q factor, not infinite

Key Principle: Resonant charging exploits the energy storage capability of inductors and capacitors. By timing the energy injection to match the natural oscillation, we can build up substantial energy in the circuit with modest input power—the same principle used in pushing a swing at just the right moment.

Next: Step-Charging Ladder Effect →


Step Charging

Step-Charging Ladder Effect

Step-charging, also known as the "staircase" or "ladder" effect, refers to the progressive buildup of voltage across a capacitor through successive resonant pulses. This technique can achieve voltage levels far beyond what single-pulse resonant charging provides.

The Concept

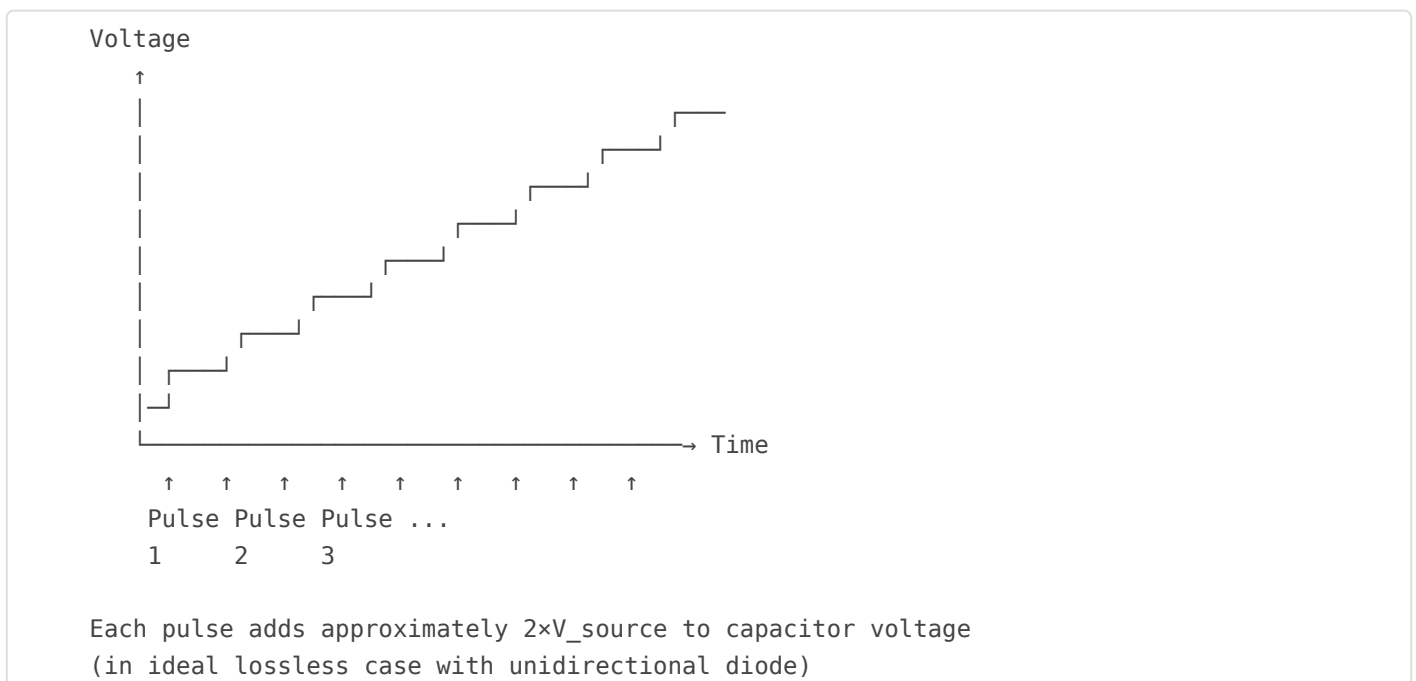Instead of maintaining continuous oscillation, step-charging applies discrete pulses that each add a quantum of energy to the capacitor. The voltage builds up incrementally:




How Step-Charging Works

Step-by-Step Process:

1. **Pulse 1:** Capacitor charges from 0 to $2V_s$ (resonant half-cycle)
2. **Hold:** Diode prevents discharge back through inductor
3. **Pulse 2:** Starting from $2V_s$, capacitor charges to $\sim 4V_s$
4. **Hold:** Energy stored, waiting for next pulse
5. **Continue:** Each pulse adds $\sim 2V_s$ (minus losses)

Circuit for Step-Charging

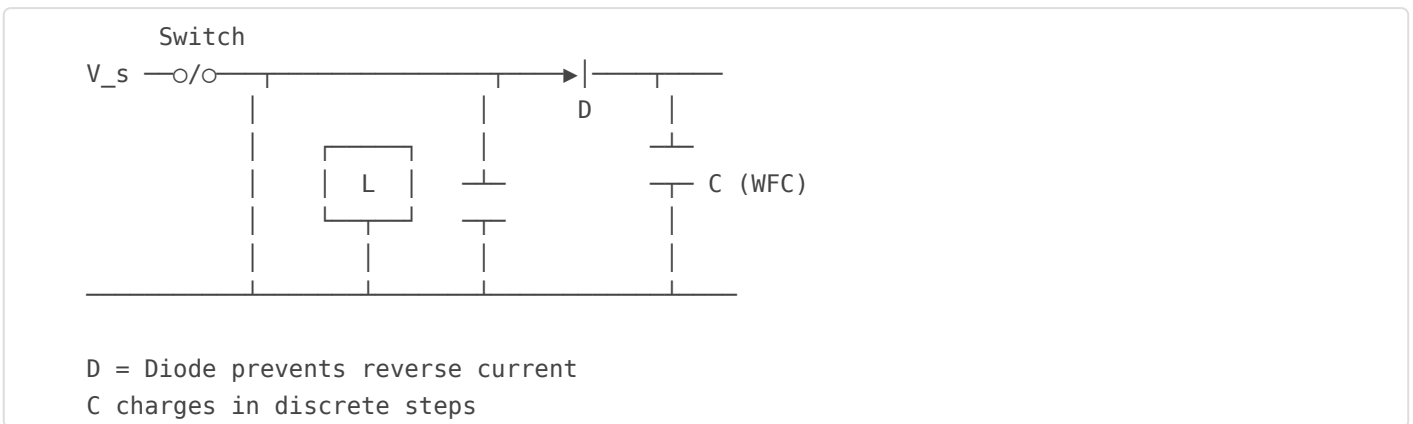

Voltage After N Pulses

Ideal Case (no losses):

$$V_{C,N} = 2N \times V_{\text{source}}$$

With Losses (exponential decay factor):

$$V_{C,N} = 2V_s \times (e^{-\pi/(2Q)})^k \text{ for } k=0 \text{ to } N-1$$

Converges to Maximum:

$$V_{C,\text{max}} = 2V_s / (1 - e^{-\pi/(2Q)})$$

$$\text{For high } Q: V_{C,\text{max}} \approx (4Q/\pi) \times V_{\text{source}}$$

Maximum Voltage vs. Q Factor

Q Factor

$V_{\text{max}}/V_{\text{source}}$

Pulses to 90%

10	~12.7	~6
20	~25.5	~12
50	~63.7	~30
100	~127	~60

Comparison: Continuous vs. Step Charging

Aspect	Continuous Resonance	Step Charging
Max voltage	$Q \times V_s$ (AC peak)	$(4Q/\pi) \times V_s$ (DC)
Waveform	Sinusoidal	Staircase
Power delivery	Constant	Pulsed
Complexity	Simpler	Needs diode/timing

Step-Charging in VIC Systems

Meyer's designs allegedly used step-charging principles:

- **Unidirectional charging:** Diode prevents energy return to source
- **Pulse timing:** Gated pulses at resonant frequency
- **Voltage accumulation:** Progressive buildup across WFC
- **Controlled discharge:** Occasional reset or bleed-off of accumulated voltage

Pulse Train Design

Optimal Pulse Parameters:

- **Pulse duration:** $\pi\sqrt{LC}$ = half resonant period

- **Pulse frequency:** $f_{\text{pulse}} < f_{\text{resonant}}/2$
- **Duty cycle:** Typically 10-50%
- **Gap between pulses:** Allow ring-down and settling

Energy Considerations

Energy Stored After N Pulses:

$$E_{C,N} = \frac{1}{2}C(V_{C,N})^2 = \frac{1}{2}C(2NV_s)^2 = 2CN^2V_s^2$$

Energy Delivered per Pulse:

$$\Delta E = E_{C,N} - E_{C,N-1} = 2CV_s^2(2N-1)$$

Each successive pulse adds more energy because it's working against a higher voltage!

Practical Implementation

Driver Circuit Requirements:

1. **High-speed switching:** MOSFET or IGBT driver
2. **Precise timing:** Microcontroller or pulse generator
3. **High-voltage diode:** Fast recovery, rated for expected voltages
4. **Voltage monitoring:** Feedback to prevent over-voltage

Safety Considerations:

- Voltages can reach dangerous levels quickly
- Energy stored in capacitor can be lethal
- Include bleed resistor for safe discharge
- Implement hardware over-voltage protection

VIC Matrix Simulation

The VIC Matrix Calculator can simulate step-charging behavior:

- **Step-charge simulation:** Predicts voltage after N pulses
- **Loss modeling:** Accounts for resistance and dielectric losses
- **Time to saturation:** How many pulses to reach maximum voltage

- **Energy efficiency:** Tracks energy delivered vs. stored

Key Insight: Step-charging combines the voltage doubling of resonant charging with the cumulative effect of multiple pulses. With sufficient Q factor, extremely high voltages can be developed across the WFC—voltages that would be impossible to achieve directly from the source.

Chapter 4 Complete. Next: Choke Design & Construction →