

# Experimental Validation

## Experimental Validation Methods

Theoretical calculations and simulations must be validated with actual measurements. This page covers practical techniques for measuring VIC circuit parameters and comparing results to predictions.

## Essential Test Equipment

Equipment	Purpose	Key Specifications
Oscilloscope	Waveform viewing, frequency measurement	2+ channels, 100+ MHz bandwidth
Function Generator	Provide test signals	1 Hz - 1 MHz, variable duty cycle
LCR Meter	Measure L, C, R	Multiple test frequencies (1 kHz, 10 kHz)
Multimeter	DC resistance, voltage	True RMS, low-ohm capability
Current Probe	Non-contact current measurement	AC/DC, appropriate bandwidth
High-Voltage Probe	Measure high voltages safely	1000:1 or 100:1, rated voltage

## Component Verification

### Measuring Inductance

Method 1: LCR Meter (Preferred)

1. Set LCR meter to inductance mode
2. Select test frequency (1 kHz typical)
3. Connect inductor, read value
4. Repeat at 10 kHz to check for frequency dependence

## Method 2: Resonance with Known C

1. Connect inductor with known capacitor C
2. Drive with function generator, sweep frequency
3. Find resonant frequency  $f_0$  (voltage peak)
4. Calculate:  $L = 1/(4\pi^2f_0^2C)$

## Measuring DCR

### Four-Wire (Kelvin) Measurement:

For accurate low-resistance measurement, use 4-wire method to eliminate lead resistance:

- Use dedicated low-ohm meter
- Or use LCR meter in R mode
- Allow reading to stabilize (self-heating)

**Expected accuracy:**  $\pm 1-5\%$  compared to calculated value

## Measuring WFC Capacitance

1. Fill WFC with water at operating temperature
2. Measure with LCR meter at 1 kHz and 10 kHz
3. Values should be similar (if EDL effects are small)
4. Note the ESR reading as well

**Expected accuracy:**  $\pm 10\text{-}20\%$  compared to calculated value

# Resonant Frequency Measurement

## Frequency Sweep Method

### Setup:

```
Function → [VIC ] → Oscilloscope
Generator [Circuit] Ch1: Input
                Ch2: Output (across WFC)
```

### Procedure:

1. Set function generator to low amplitude sine wave
2. Start at low frequency (1/10 of expected  $f_0$ )
3. Slowly increase frequency while watching Ch2 amplitude
4. Note frequency of maximum amplitude—this is  $f_0$
5. Also note -3dB frequencies (where amplitude =  $0.707 \times$  peak)

### Calculate Q from Measurement:

$$Q = f_0 / (f_{\text{high}} - f_{\text{low}}) = f_0 / \text{BW}$$

# Phase Measurement Method

1. Display both input current and output voltage
2. Use X-Y mode or measure phase with oscilloscope
3. At resonance, phase difference =  $0^\circ$
4. More accurate than amplitude peak for high-Q circuits

# Q Factor Measurement

## Method 1: Bandwidth

Measure -3dB bandwidth and calculate:

$$Q = f_0 / BW$$

## Method 2: Ring-Down

1. Excite circuit with single pulse at  $f_0$
2. Observe decaying oscillation on oscilloscope
3. Count cycles to decay to  $1/e$  (37%)
4.  $Q \approx \pi \times (\text{number of cycles to } 1/e \text{ decay})$

Alternatively, measure time constant  $\tau$ :

$$\tau = 2L/R = Q / (\pi f_0)$$

## Method 3: Voltage Magnification

1. Measure input voltage  $V_{in}$
2. Measure output voltage  $V_{out}$  at resonance
3.  $Q \approx V_{out}/V_{in}$

**Caution:** This assumes lossless input coupling. Actual Q may be higher due to source impedance effects.

## Comparing Calculated vs. Measured

Parameter	Acceptable Difference	If Larger Difference
Inductance	$\pm 20\%$	Check core $\mu_r$ , turn count
DCR	$\pm 10\%$	Check wire gauge, connections
WFC Capacitance	$\pm 20\%$	Check geometry, water level
Resonant Frequency	$\pm 15\%$	Check L and C values
Q Factor	$\pm 30\%$	Look for missing losses

## Troubleshooting Discrepancies

Measured f? Lower than Calculated:

- Stray capacitance adding to total C
- Actual L higher than calculated
- Check for loose connections (add L)

## Measured f? Higher than Calculated:

- Actual L lower (core saturation, wrong  $\mu_r$ )
- WFC capacitance overestimated
- Air bubbles reducing effective C

## Measured Q Lower than Calculated:

- Additional losses not accounted for
- Core losses at operating frequency
- Poor connections adding resistance
- Radiation losses at high frequency

## No Clear Resonance Observed:

- Operating above SRF (choke is capacitive)
- Very low Q ( $Q < 2$ ) makes resonance hard to see
- Measurement setup loading the circuit

# Documentation Template

## Record for Each Test:

Date: \_\_\_\_\_

Circuit ID: \_\_\_\_\_

COMPONENT VALUES (Calculated / Measured):

L1: \_\_\_\_\_ mH / \_\_\_\_\_ mH  
L2: \_\_\_\_\_ mH / \_\_\_\_\_ mH  
DCR1: \_\_\_\_\_  $\Omega$  / \_\_\_\_\_  $\Omega$   
DCR2: \_\_\_\_\_  $\Omega$  / \_\_\_\_\_  $\Omega$   
C\_wfc: \_\_\_\_\_ nF / \_\_\_\_\_ nF  
C1: \_\_\_\_\_ nF / \_\_\_\_\_ nF

RESONANCE (Calculated / Measured):  
f<sub>o</sub>\_primary: \_\_\_\_\_ kHz / \_\_\_\_\_ kHz  
f<sub>o</sub>\_secondary: \_\_\_\_\_ kHz / \_\_\_\_\_ kHz

PERFORMANCE (Calculated / Measured):  
Q: \_\_\_\_\_ / \_\_\_\_\_  
Bandwidth: \_\_\_\_\_ Hz / \_\_\_\_\_ Hz  
V\_magnification: \_\_\_\_\_ / \_\_\_\_\_

NOTES:  
\_\_\_\_\_

# Safety Considerations

## ?? High Voltage Warning:

- VIC circuits can develop high voltages at resonance
- Always use proper high-voltage probes
- Keep one hand in pocket when probing live circuits
- Discharge capacitors before handling

## ?? Gas Production:

- WFC produces hydrogen and oxygen—ensure ventilation
- No open flames or sparks near operating cell
- Use appropriate gas collection if needed

**Best Practice:** Always compare measured values to calculator predictions. This builds confidence in both your construction skills and the calculator's accuracy. Document discrepancies—they often

reveal important lessons about real-world effects.

*Chapter 8 Complete. See Appendices for reference tables and formulas. →*

---

Revision #1

Created 2026-01-01 20:47:12 UTC by Chris Bake

Updated 2026-01-01 20:47:24 UTC by Chris Bake