


Randles Circuit

The Randles Equivalent Circuit

The Randles circuit is the most widely used equivalent circuit model for electrochemical interfaces. It captures the essential elements of an electrode-electrolyte system and serves as the foundation for more complex models used in WFC analysis.

The Classic Randles Circuit

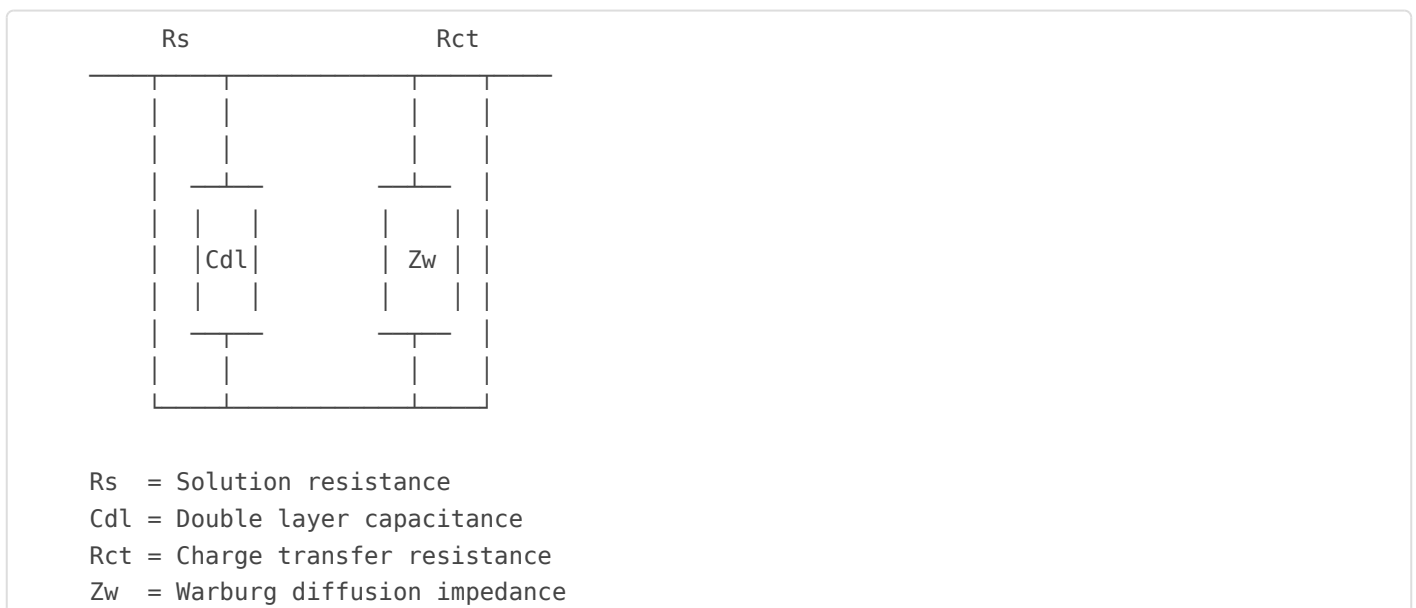Proposed by John Randles in 1947, this circuit combines resistive, capacitive, and diffusion elements:



Component Meanings

Element	Physical Origin	Typical Value (WFC)
R_s	Ionic resistance of electrolyte solution between electrodes	10 Ω - 10 k Ω (depends on conductivity)

Element	Physical Origin	Typical Value (WFC)
C_{dl}	Electric double layer capacitance at electrode surface	μF to mF range (depends on area)
R_{ct}	Resistance to electron transfer at electrode (reaction kinetics)	1Ω - $1 \text{M}\Omega$ (depends on overpotential)
Z_w	Impedance due to diffusion of reactants/products	Frequency-dependent (see Warburg page)

Total Impedance

The total impedance of the Randles circuit is:


$$Z_{total} = R_s + [Z_{Cd1} || (R_{ct} + Z_w)]$$

Expanding:

$$Z_{total} = R_s + [(R_{ct} + Z_w)] / [1 + j\omega C_{dl}(R_{ct} + Z_w)]$$

Frequency Response

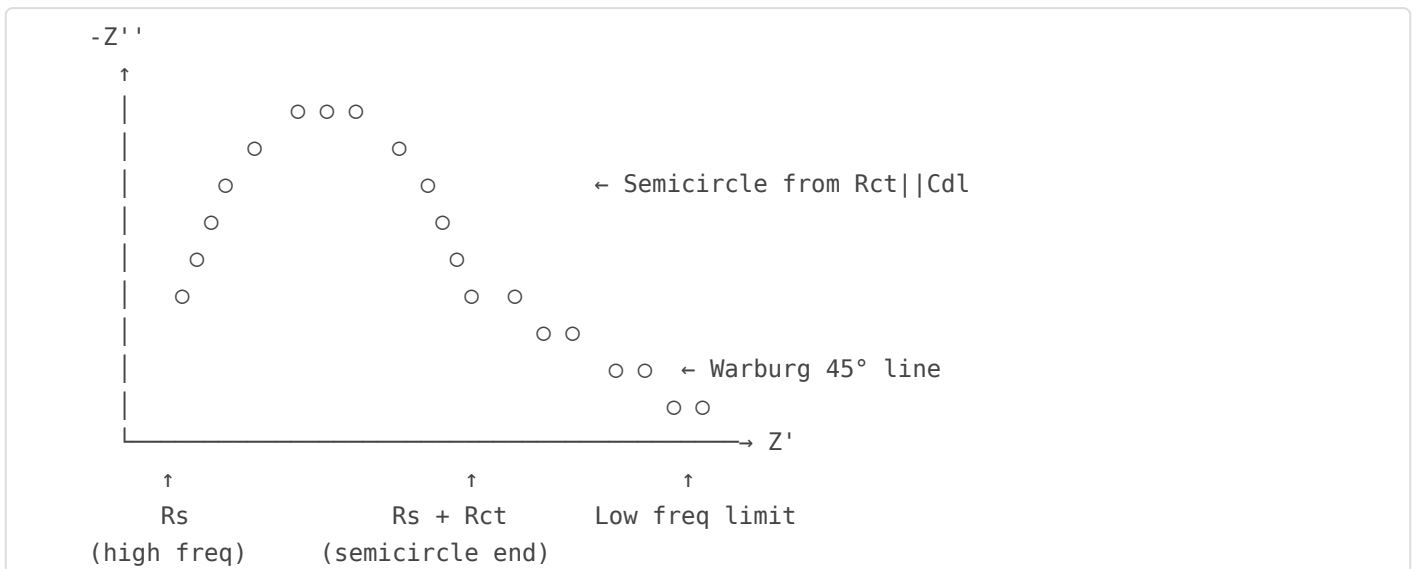The Randles circuit produces a characteristic Nyquist plot:



Time Constants in the Randles Circuit

Double Layer Time Constant:

$$\tau_{dl} = R_s \times C_{dl}$$

Determines how quickly the double layer charges through the solution resistance.

Charge Transfer Time Constant:

$$\tau_{ct} = R_{ct} \times C_{dl}$$

Determines the peak frequency of the semicircle: $f_{peak} = 1/(2\pi\tau_{ct})$

Simplified Cases

Case 1: Fast Kinetics ($R_{ct} \rightarrow 0$)

When the electrochemical reaction is very fast:

- Semicircle disappears
- Only Warburg tail remains at low frequency
- The system is "diffusion-controlled"

Case 2: Slow Kinetics ($R_{ct} \rightarrow \text{large}$)

When the electrochemical reaction is slow:

- Large semicircle dominates
- Warburg region may not be visible
- The system is "kinetically-controlled"

Case 3: No Faradaic Reaction ($R_{ct} \rightarrow \infty$)

When no electrochemical reaction occurs (blocking electrode):

- No semicircle
- Purely capacitive behavior at low frequency
- Nyquist plot is a vertical line


Randles Circuit for WFC

In a water fuel cell, the Randles elements have specific meanings:

Element	WFC Interpretation	Effect on VIC
R_s	Water conductivity, electrode gap	Adds to total circuit resistance, reduces Q
C_{dl}	EDL at each electrode	Part of total WFC capacitance
R_{ct}	Activation barrier for water splitting	Limits DC current, less relevant at high freq
Z_w	Diffusion of H_2/O_2 gases, ions	Important at low frequencies only

Extended Randles Circuit

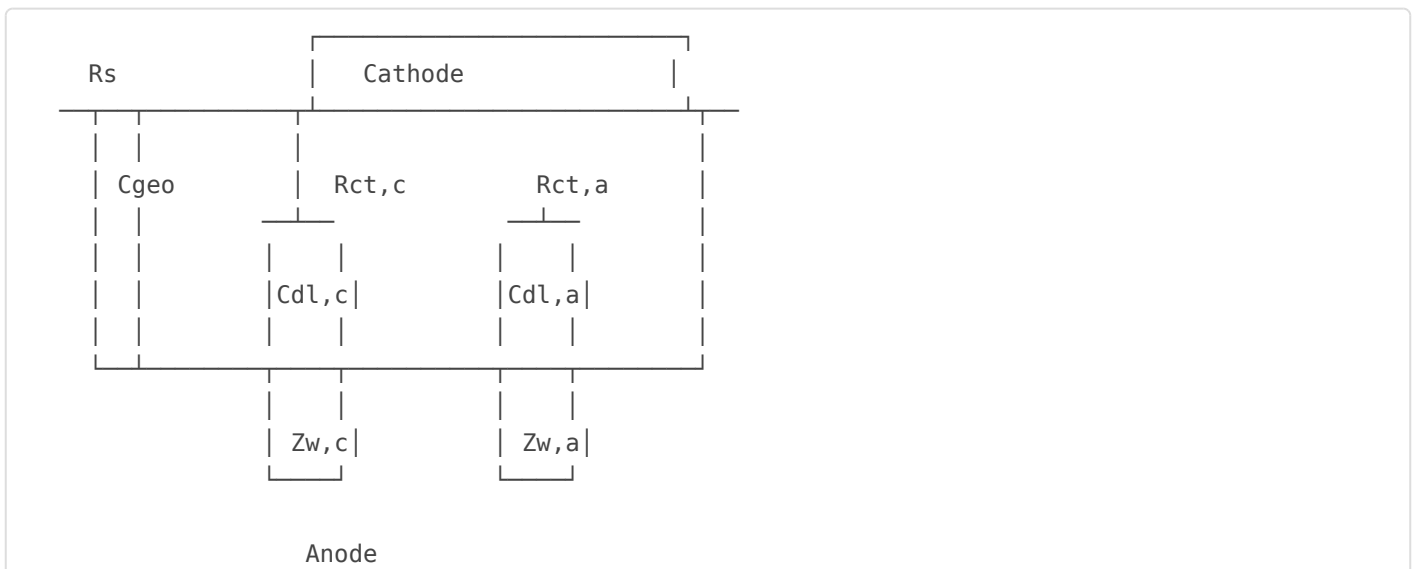For more accurate WFC modeling, the Randles circuit can be extended:



This model includes separate elements for anode and cathode interfaces plus the geometric capacitance.

Parameter Extraction

From an experimental EIS measurement, Randles parameters can be extracted:

1. R_s : High-frequency real-axis intercept
2. R_{ct} : Diameter of the semicircle
3. C_{dl} : From peak frequency: $C = 1/(2\pi f_{peak} R_{ct})$
4. **Warburg coefficient**: From slope of the 45° line

Software Tools: Programs like ZView, EC-Lab, and Nova can automatically fit Randles parameters to EIS data. Open-source options include impedance.py (Python) and EIS Spectrum Analyzer.

VIC Design Application: The Randles circuit shows that at VIC operating frequencies (1-50 kHz), the WFC behaves primarily as C_{dl} in series with R_s . The charge transfer resistance and Warburg impedance become important only at lower frequencies where actual water splitting occurs.

Next: Cole-Cole Relaxation Model →

Revision #1

Created 2026-01-01 20:38:23 UTC by Chris Bake

Updated 2026-01-01 20:38:34 UTC by Chris Bake