




CrayonXA (My First 9XA)

Learning transistors, power supplies, 555 timers, Schmidt Triggers, AND gates, darlington transistors and optocouplers all in one shot. It still amazes me this ever worked :)

The circuit for this design originated from [Max Miller's 9XA](#) (drawn in crayon)

Max Millers' 9XA 

A funny video illustrating how I still had much to learn about building circuits :)

<https://www.youtube.com/embed/2tQNh7vZGUA?t=7s>

More progress on the 9XA. Learning how proper transistor biasing and loading is important for controlling amplitude modulation.

<https://www.youtube.com/embed/GF0GO3bbr0s>

Revision #8

Created 25 June 2022 23:40:03 by Chris Bake

Updated 26 June 2022 03:35:08 by Chris Bake