

# LC VOLTAGE

The impedance of an inductor and a capacitor in series,  $Z_{\text{series}}$ , is given by

The impedance of an inductor and a capacitor in series,  $Z_{\text{series}}$  is given by

$$Z_{\text{series}} = (X_C - X_L)$$

Where

$$X_C = \frac{1}{2\pi FC}$$

$$X_L = 2\pi FL$$

The Resonant Frequency (F) of an LC circuit in series is given by

$$F = \frac{1}{2\pi \sqrt{LC}}$$

Ohm's Law for LC circuit in series is given by

$$V_T = IZ$$

$$Z_{\text{series}} = (X_C - X_L)$$

Where

$$X_C = 1 / 2(\pi)FC$$

The **Resonant Frequency (F)** of an LC circuit in series is given by


The Resonant Frequency (F) of an LC circuit in series is given by

$$F = \frac{1}{2\pi \sqrt{LC}}$$

**Ohm's Law** for an LC circuit in series is given by

$$V_t = IZ$$

## LC VOLTAGE

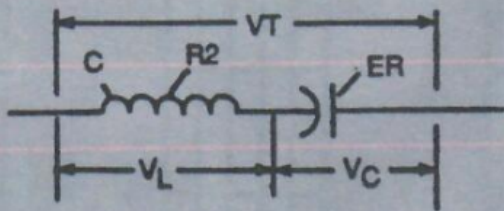

**FIGURE 1 - 2. LC CIRCUIT SCHEMATIC**

The voltage across the **inductor** (c) or

**capacitor** (ER of t) is greater than the **applied voltage** (h).

At frequency close to resonance, the voltage across the individual components is higher than the **applied voltage** (h), and, at resonant frequency, the voltage VT across both the inductor and the capacitor are theoretically infinite.

However, physical constraints of components and circuit interaction prevent the voltage from reaching infinity.

The **voltage** (VL) across the **inductor** (C) is given by the equation:

The voltage (VL) across the inductor (C) is given by the equation

$$V_L = \frac{V_T X_L}{(X_L - X_C)}$$

Revision #2

Created 26 October 2024 15:12:27 by Chris Bake

Updated 26 October 2024 15:24:49 by Chris Bake