

RLC Circuit

Inductor (C) is made of or composed of **resistive wire** (R2) to further restrict D.C. current flow beyond inductance reaction (XL), and, is given by

(Eq 8)

$$Z = \sqrt{R_I^2 + (X_l - X_c)^2}$$

Revision #1

Created 19 December 2023 18:32:22 by Chris Bake

Updated 20 December 2023 04:43:51 by Chris Bake